

Figure 2–1. Cyclone II EP2C20 Device Block Diagram

 


Figure 2–2. Cyclone II LE

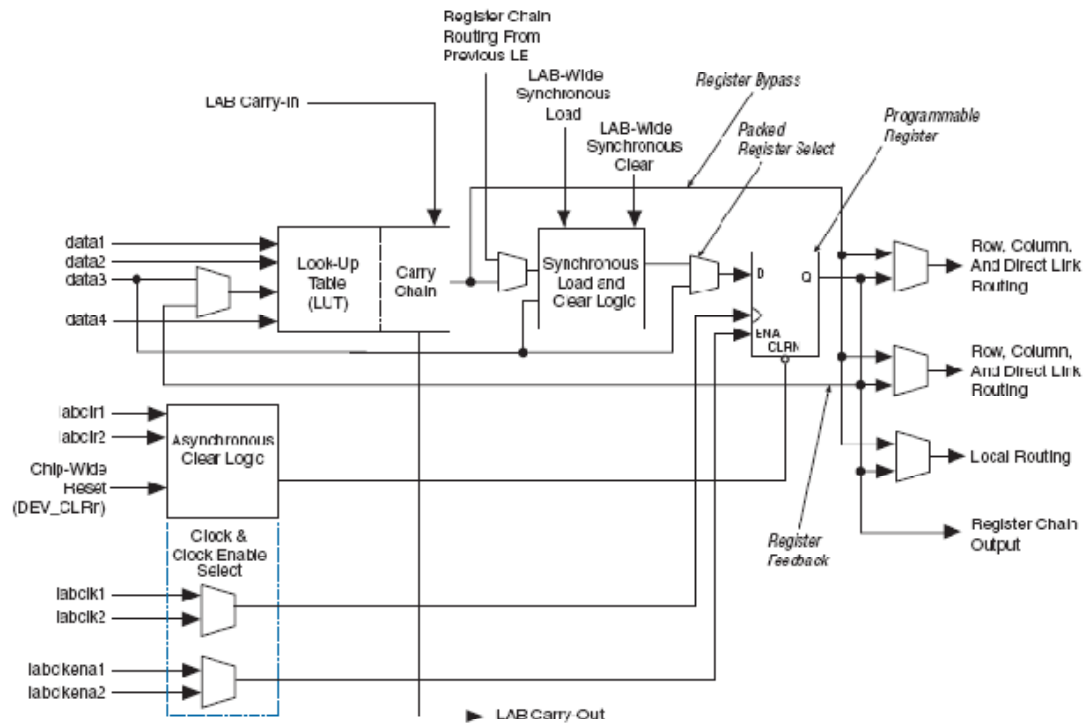


Figure 2-3. LE in Normal Mode

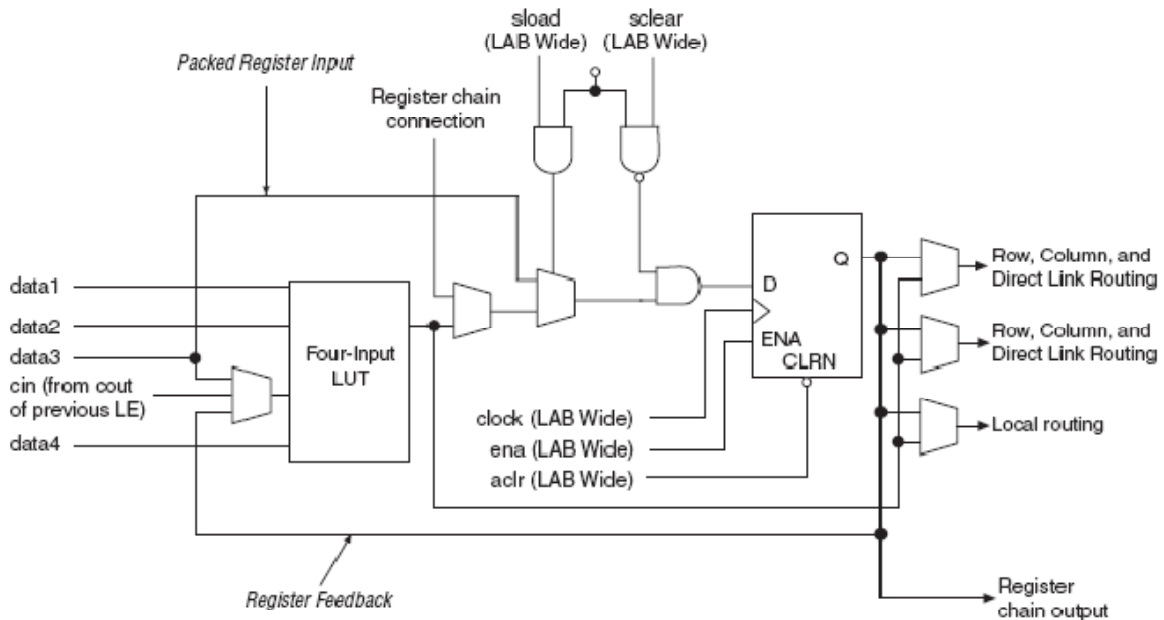


Figure 2-4. LE in Arithmetic Mode

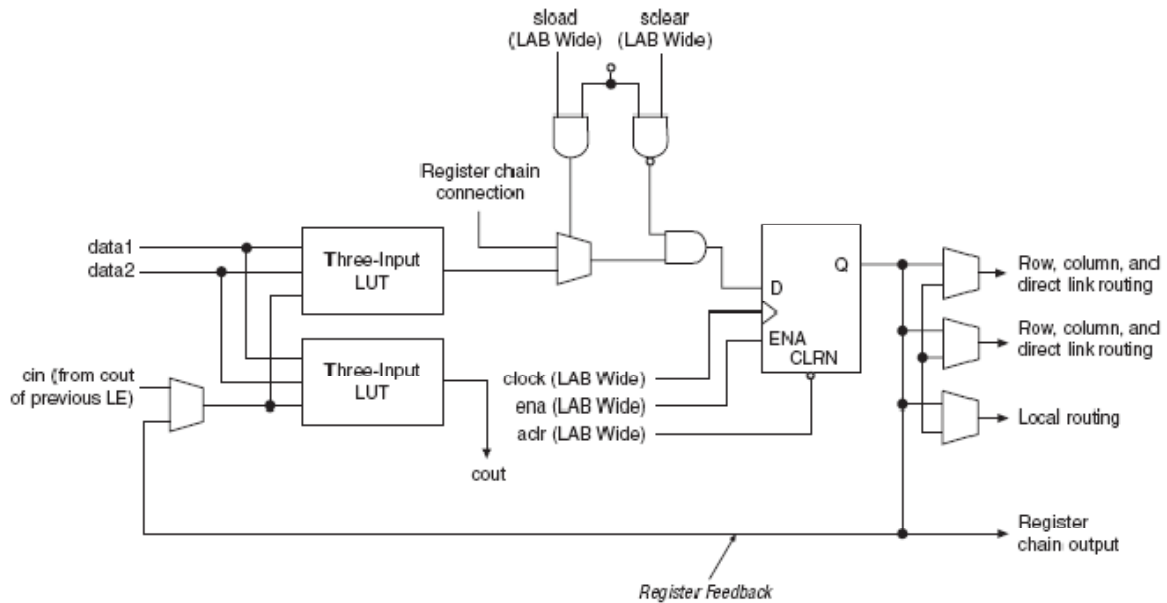


Figure 2-5. Cyclone II LAB Structure

 


Figure 2-6. Direct Link Connection

 


Figure 2-7. LAB-Wide Control Signals


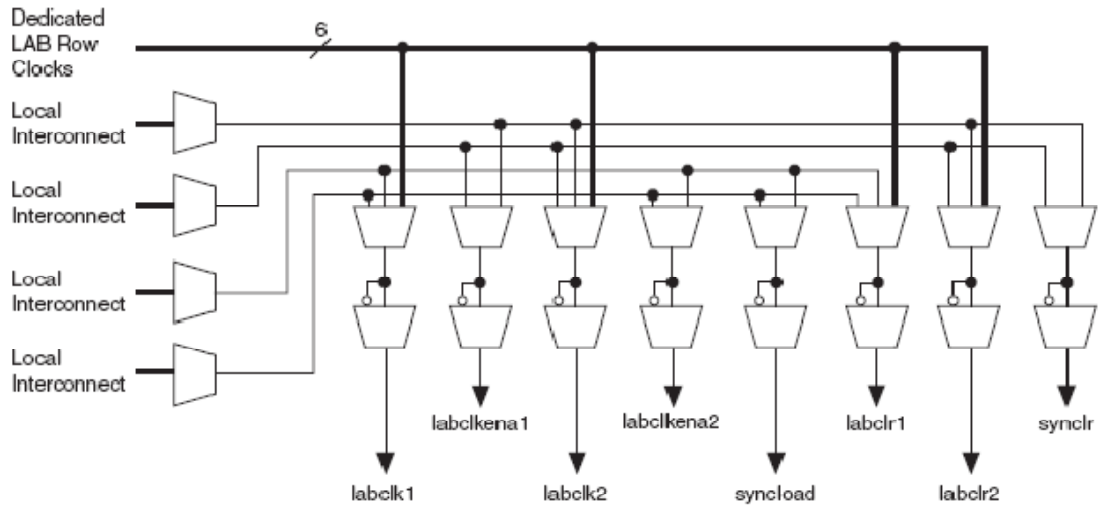


Figure 2–8. R4 Interconnect Connections

 

Notes to Figure 2–8:

- (1) C4 interconnects can drive R4 interconnects.
- (2) This pattern is repeated for every LAB in the LAB row.

Figure 2-9. Register Chain Interconnects


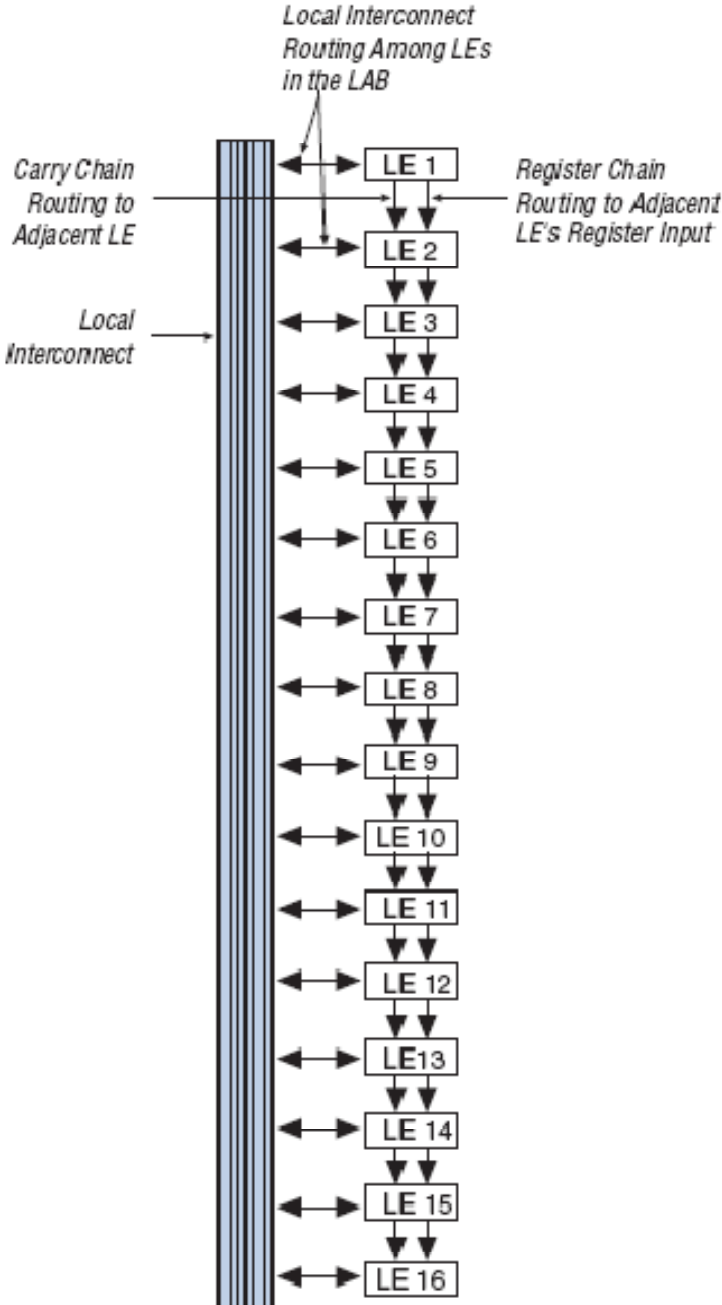


Figure 2-10. C4 Interconnect Connections *Note (1)*

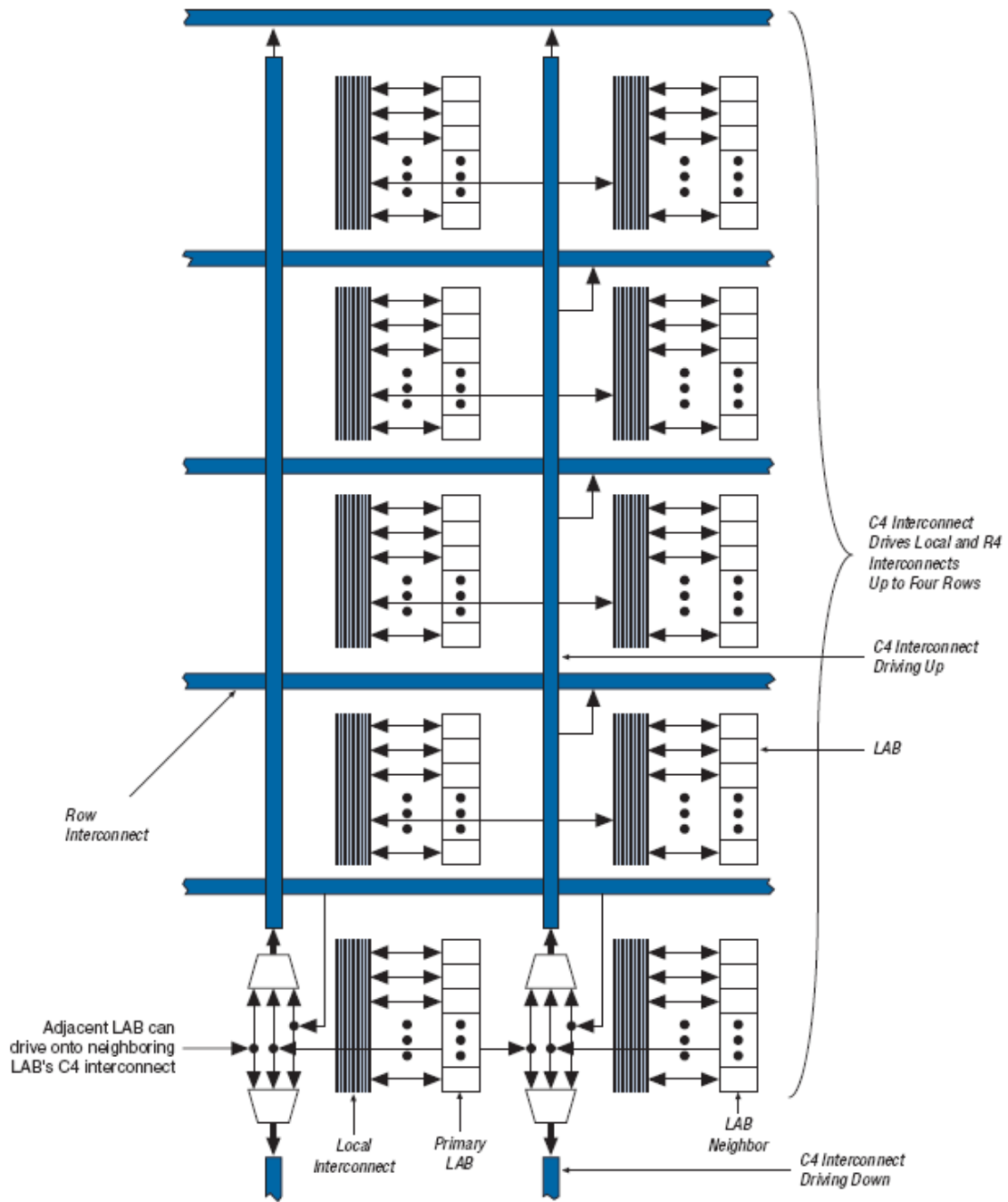

Note to Figure 2-10:

- (1) Each C4 interconnect can drive either up or down four rows.

Figure 2-17. M4K RAM Block LAB Row Interface


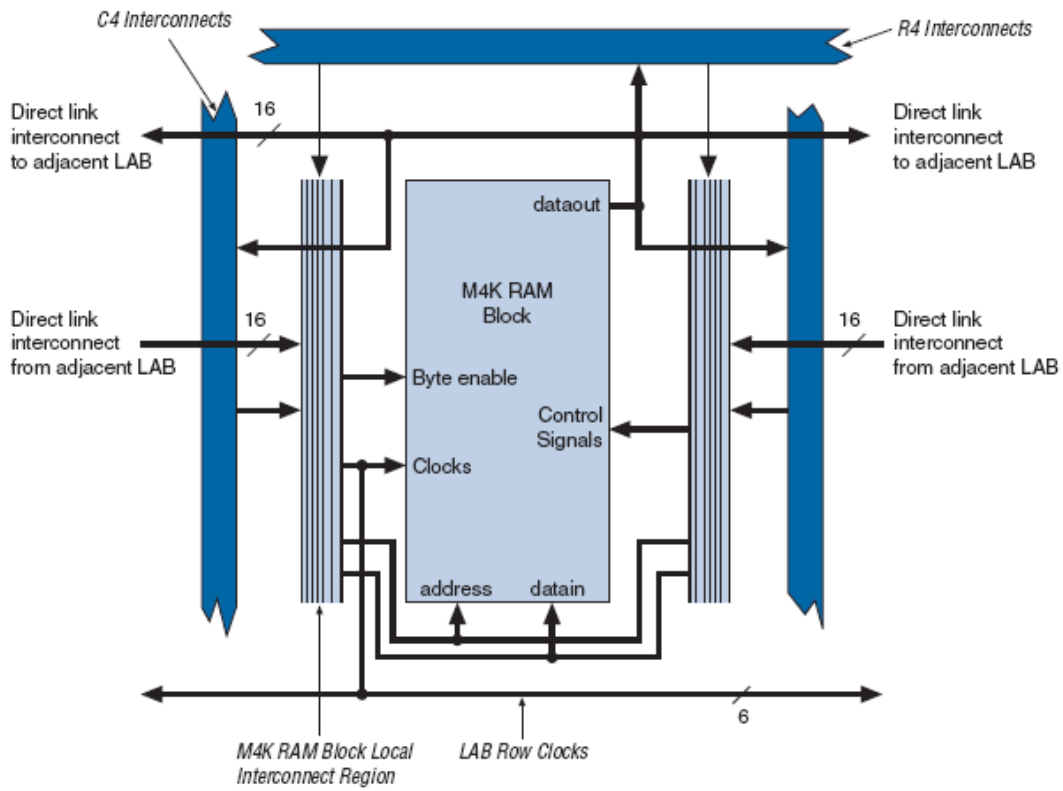


Figure 2-18. Multiplier Block Architecture

 

Note to Figure 2-18:

- (1) If necessary, these signals can be registered once to match the data signal path.

Figure 2-19. Embedded Multiplier LAB Row Interface


 



Figure 2-21. Row I/O Block Connection to the Interconnect

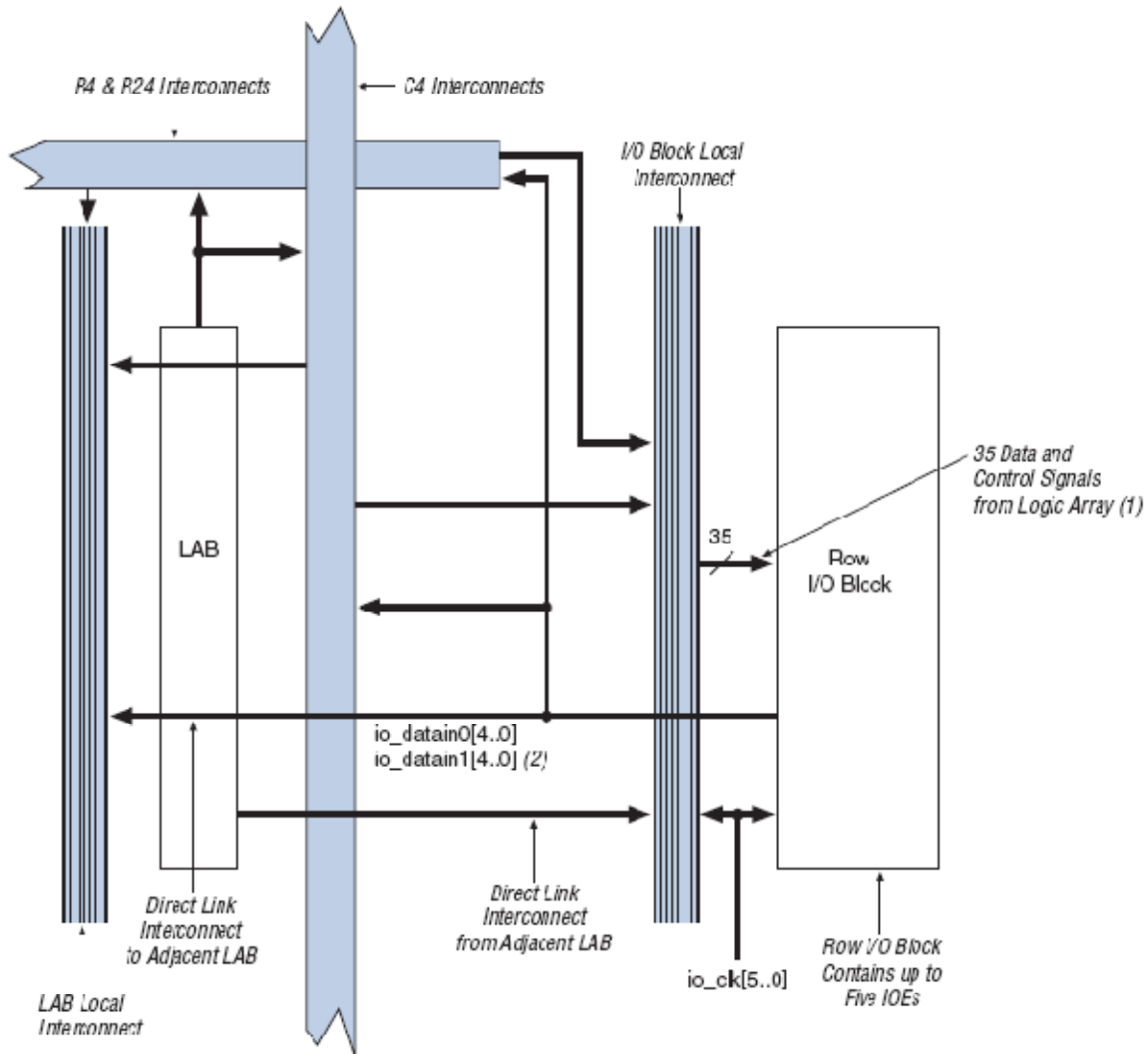

Notes to Figure 2-21:

- (1) The 35 data and control signals consist of five data out lines, $io_dataout[4..0]$, five output enables, $io_coe[4..0]$, five input clock enables, $io_cce_in[4..0]$, five output clock enables, $io_cce_out[4..0]$, five clocks, $io_clk[4..0]$, five asynchronous clear signals, $io_caclr[4..0]$, and five synchronous clear signals, $io_scclr[4..0]$.
- (2) Each of the five IOEs in the row I/O block can have two io_datain (combinational or registered) inputs.

Figure 2–22. Column I/O Block Connection to the Interconnect

 

Notes to Figure 2–22:

- (1) The 28 data and control signals consist of four data out lines, $io_dataout[3..0]$, four output enables, $io_coe[3..0]$, four input clock enables, $io_cce_in[3..0]$, four output clock enables, $io_cce_out[3..0]$, four clocks, $io_clk[3..0]$, four asynchronous clear signals, $io_cac1r[3..0]$, and four synchronous clear signals, $io_csc1r[3..0]$.
- (2) Each of the four IOEs in the column I/O block can have two io_datain (combinational or registered) inputs.