

IMPORTANT:

- Please be neat and write (or draw) carefully throughout the test. If we cannot read it with a reasonable effort, it is assumed wrong.
- As always, the best answer gets the most points.

1. Miscellaneous.

(a) Clock debouncing using a shift register and a clock divider

10 pts.


Design a switch debouncing circuit using a clock divider and a shift register (with an AND gate) with the following assumptions:

- The bouncing period of a switch is determined to be 8 milli-seconds.
- The system clock is 20 MHz
- The clock divider is designed using 16 flip-flops.

What is the minimum number of flip-flops can be used for the shift register that will “cover” the bounding period of the switch?

(For credit, show work here.) _____ (answer) (5 pts.)

(b) VGA display calculation:

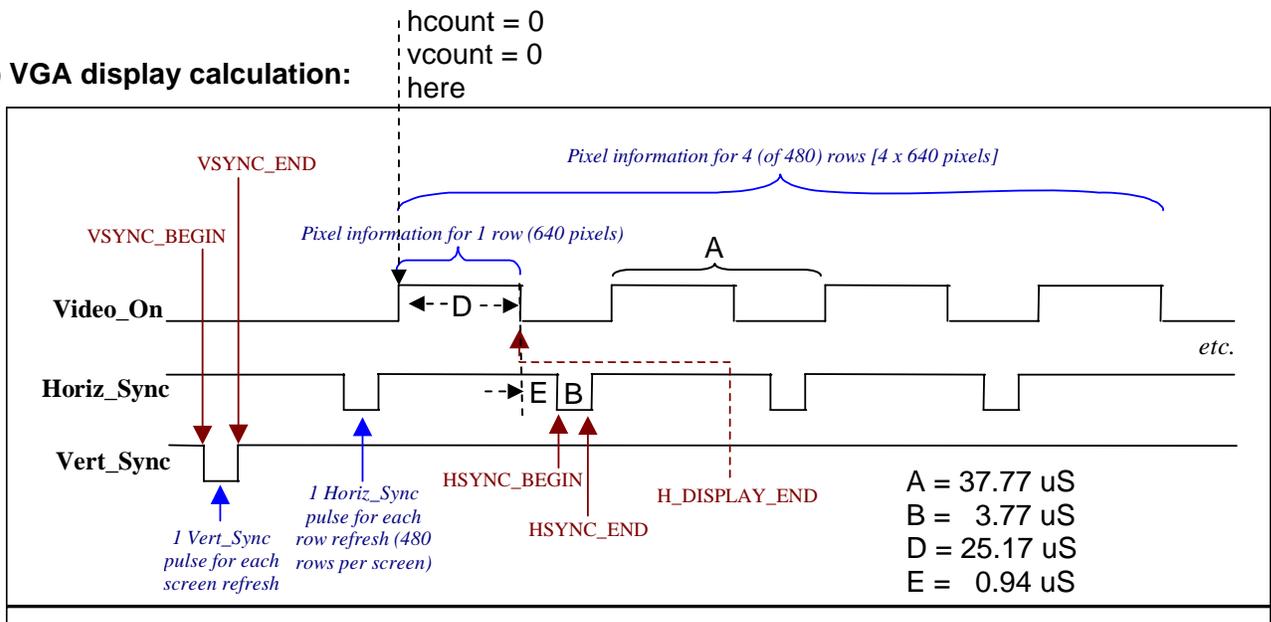


For Lab 5, assuming the board clock frequency is 20 MHz, what constant should be use for HSYNC_END? For credit, please show work.

(For credit, show work here.) _____ (answer) (5 pts.)

18 pts.

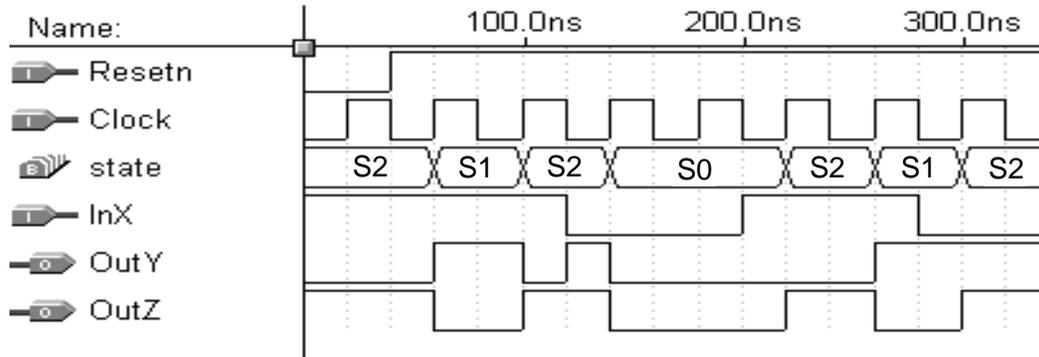2. **ASM/VHDL.** Given below is a timing diagram (functional simulation) showing the desired timings among the states and signals of a controller.



(a) Construct an ASM diagram that will produce the above behavior. (8 pts.)

(b) Complete the VHDL specification (on the next page) of your ASM diagram. Please don't change the structure of the code. In other words, **you have to use the second CASE statement** to implement the conditional and unconditional outputs. (10 pts.)

```

ENTITY Test2P2 IS
    PORT ( Clock, Resetn, InX      : IN   STD_LOGIC ; -- Resetn is active low, asynchronous
          OutY, OutZ              : OUT  STD_LOGIC );
END Test2P2;
    
```

2(b) ARCHITECTURE ASMArch OF Test2P2 IS

TYPE ASMstateType IS (S0, S1, S2) ; -- User defined signal type
SIGNAL state : ASMstateType ;

BEGIN

PROCESS () -- state transitions

BEGIN

IF Resetn = '0' THEN

ELSIF () THEN

CASE state IS

WHEN S0 =>

WHEN S1 =>

WHEN S2 =>

END CASE ;

END IF ;

END PROCESS ;

PROCESS () -- conditional and uncond. outputs

BEGIN

CASE state IS – You have to use this CASE statement for the outputs.

WHEN S0 =>

WHEN S1 =>

WHEN S2 =>

END CASE ;

END PROCESS ;

END ASMArch ;

17 pts.

3. **VHDL / ASM.** Given the VHDL specification, draw the corresponding ASM chart. (Put ASM chart on the next page.)

ENTITY Prob3 IS

```
PORT ( Clock, ResetA, ResetB, EN : IN  STD_LOGIC ;
      RegLD, WE, SEL      : OUT  STD_LOGIC ) ;
```

END Prob3 ;

ARCHITECTURE ASMArch OF Prob3 IS

```
SIGNAL state : STD_LOGIC_Vector (1 DOWNT0 0);
CONSTANT A : STD_LOGIC_Vector (1 DOWNT0 0):= "01";
CONSTANT B : STD_LOGIC_Vector (1 DOWNT0 0):= "11";
CONSTANT C : STD_LOGIC_Vector (1 DOWNT0 0):= "00";
CONSTANT D : STD_LOGIC_Vector (1 DOWNT0 0):= "10";
```

BEGIN

PROCESS (state, ResetB, EN)

BEGIN

```
    RegLD <= '0';
```

```
    WE <= '0';
```

```
    CASE state IS
```

```
        WHEN A =>
```

```
            IF ResetB = '1' AND EN = '1' THEN RegLD <= '1'; END IF;
```

```
        WHEN B =>
```

```
            RegLD <= '1';
```

```
        WHEN C =>
```

```
            RegLD <= '1';
```

```
            IF ResetB = '0' AND EN = '1' THEN WE <= '1'; END IF;
```

```
        WHEN OTHERS =>
```

```
    END CASE ;
```

END PROCESS ;

```
SEL <= '1' WHEN (state = "11") OR (state = "00" AND ResetB = '0' AND EN = '0') ELSE '0';
```

PROCESS (ResetA, Clock) -- State transitions

BEGIN

```
    IF ResetA = '0' THEN
```

```
        state <= B ;
```

```
    ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
        CASE state IS
```

```
            WHEN A =>
```

```
                IF ResetB = '1' THEN state <= A ;
```

```
                ELSIF EN = '0' THEN state <= C;
```

```
                ELSE state <= "11" ;
```

```
                END IF ;
```

```
            WHEN B =>
```

```
                IF ResetB = '1' THEN state <= A ;
```

```
                ELSE state <= "10";
```

```
                END IF;
```

```
            WHEN "00" =>
```

```
                IF ResetB = '1' THEN state <= A;
```

```
                ELSE state <= D;
```

```
                END IF ;
```

```
            WHEN D =>
```

```
                state <= A;
```

```
            WHEN OTHERS =>
```

```
                state <= A;
```

```
        END CASE ;
```

```
    END IF ;
```

END PROCESS ;

END ASMArch ;

3. (Continued)


(a) Put the ASM chart for Problem 3 here. (15 pts.)

(b) Is ResetA synchronous or asynchronous? (circle one) (1 pt.)

Is ResetB synchronous or asynchronous? (circle one) (1 pt.)

4. AltSynRam Problem

17 pts.

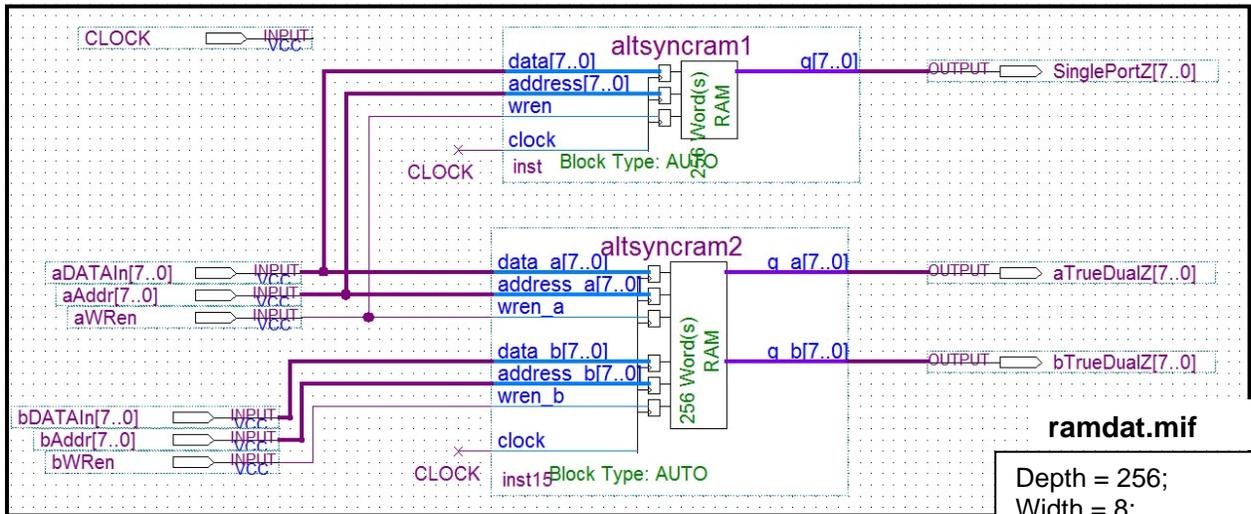


ramdat.mif

```

    Depth = 256;
    Width = 8;
    Address_radix = hex;
    Data_radix = hex;
    Content
    Begin
    00 : 70;    07 : 77;
    01 : 71;    08 : 78;
    02 : 72;    09 : 79;
    03 : 73;    0A : 7A;
    04 : 74;    0B : 7B;
    05 : 75;    0C : 7C;
    06 : 76;    etc.
    End
    
```

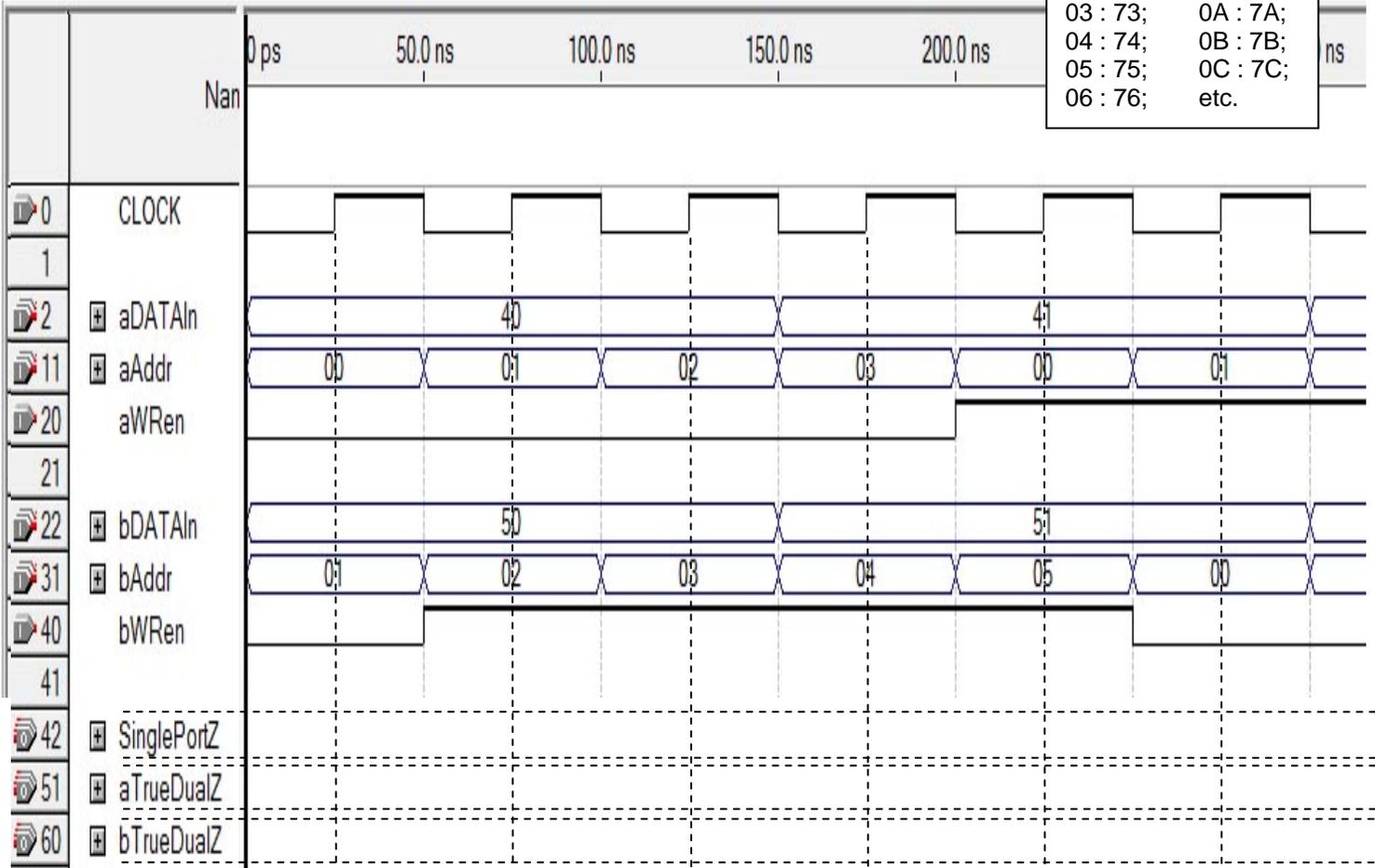
Complete the following timing diagram.
Assume all flip-flops are initialized to '0'.
 Both RAM's has the same data (ramdat.mif).



Please put **values in hex** and an "X" where the value changes for SinglePortZ, aTrueDualZ, and bTrueDualZ.

5. FIR filter ASM problem

20 pts.

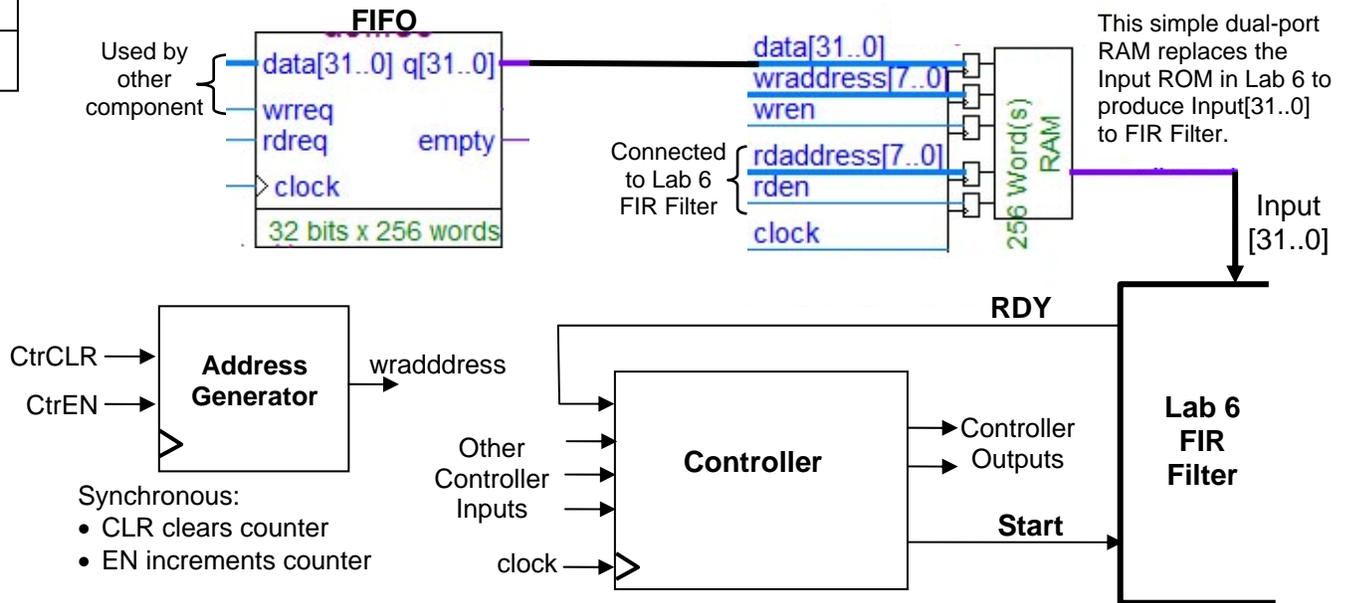

You are to design the **controller** of following component to fill the Input RAM for a Lab 6 FIR filter (from Location 0 to Location 256). Note that the Input RAM plays the same role as the Input ROM in Lab 6.

- The controller will wait until it receives a RDY = '1' from the Lab 6 FIR filter, then it will proceed to fill the Input RAM.
 - It will check to see if the FIFO is empty
 - If empty = '1', it will wait.
 - If empty = '0',
 - It will request a 32-bit value from the FIFO (set rdreq = '1'). The next value in the FIFO will be outputted from the FIFO q[31..0] at the next active clock transition.
 - This value should be written into the next location in the Input RAM.
 - This will be done until the Input RAM is full (256 locations), each time making sure the FIFO is not empty.
- When finished, it will signal the Lab 6 FIR filter by setting Start = '1' and return to the Wait state.

Note:

Function of the FIFO:

- rdreq:
 - 0: The output q[31..0] will hold the last value outputted from the FIFO.
 - 1: The next value in the FIFO will be outputted from the FIFO q[31..0] at the next active clock transition.
- empty:
 - 0: The FIFO is not empty (there are some values in it).
 - 1: The FIFO is empty.

5. continued

(a) Complete the block diagram of the Controller, specifying all the Controller inputs and Controller outputs. (4 pts.)

(b) Put the ASM chart for the Controller here. (16 pts.)

6. FIR filter Datapath component, using GENERATE statement

18 pts.

- (a) Shown on the next page is the example code that we discussed in class. Modify the code to make it into a set of 32 multipliers. You can make the changes right on the code on the next page. (6 pts.)
- You can assume that `coeff(32 DOWNT0 1)` have been defined and assigned for you to use.
- (b) Assume that we want to complete the 32-bit Datapath component, give me the code required to implement the required 32-bit shift registers to produce `reg(32 DOWNT0 1)`. (6 pts.)
- Restriction: **You cannot use PORT MAP statements for this part.** (Hint: PROCESS statement)
- (Put your answer here, including any new TYPE or SIGNAL definitions)

- (c) Continuing with the 32-bit Datapath component, give me the code required to implement the NEXT level of adders (i.e., you don't have to implement the other levels of adders). (6 pts.)
- Restriction: This time, **you have to GENERATE and PORT MAP statements for this part.**
- (Put your answer here, including any new TYPE or SIGNAL definitions)

-- snippet of code to demonstrate Multi-dimensional arrays and GENERATE statement
ARCHITECTURE struct OF datapath IS

-- Definition of other components

COMPONENT multiplier IS

```
    PORT ( clock : IN STD_LOGIC;  
          dataa : IN STD_LOGIC_VECTOR(31 DOWNT0 0);  
          datab : IN STD_LOGIC_VECTOR(31 DOWNT0 0);  
          result: OUT STD_LOGIC_VECTOR(31 DOWNT0 0) );
```

END COMPONENT;

COMPONENT adder IS

```
    PORT ( clock      : IN STD_LOGIC ;  
          dataa       : IN STD_LOGIC_VECTOR (31 DOWNT0 0);  
          datab       : IN STD_LOGIC_VECTOR (31 DOWNT0 0);  
          result      : OUT STD_LOGIC_VECTOR (31 DOWNT0 0) );
```

END COMPONENT;

SUBTYPE signalVectors IS STD_LOGIC_VECTOR(31 DOWNT0 0);

TYPE array4OfSignals IS ARRAY(4 DOWNT0 1) OF signalVectors;

TYPE array5OfSignals IS ARRAY(5 DOWNT0 1) OF signalVectors;

SIGNAL coeff: array32OfSignals; -- You can assume that coeff(32 DOWNT0 1) have
-- been defined and assigned for you to use.

SIGNAL reg: array5OfSignals; -- reg(4 DOWNT0 1) are outputs of the 4 registers
-- reg(5) is the input to the left-most registers

SIGNAL mout: array4OfSignals;

BEGIN

-- shift register code

mults: FOR i IN 1 to 4 GENERATE

```
    multArray : multiplier PORT MAP (clock=>clk, dataa=>coeff(i),  
                                     datab=>reg(i), result=>mout(i));
```

END GENERATE mults;

-- code for adders

END struct;

```
ENTITY __entity_name IS  
    PORT(__input_name, __input_name      : IN  STD_LOGIC;  
          __input_vector_name           : IN  STD_LOGIC_VECTOR(__high downto __low);  
          __bidir_name, __bidir_name     : INOUT STD_LOGIC;  
          __output_name, __output_name   : OUT  STD_LOGIC);  
END __entity_name;
```

```
ARCHITECTURE a OF __entity_name IS  
    SIGNAL __signal_name : STD_LOGIC;  
    SIGNAL __signal_name : STD_LOGIC;  
BEGIN  
    -- Process Statement  
    -- Concurrent Signal Assignment  
    -- Conditional Signal Assignment  
    -- Selected Signal Assignment  
    -- Component Instantiation Statement  
END a;
```

```
__instance_name: __component_name PORT MAP (__component_port => __connect_port,  
                                               __component_port => __connect_port);
```

```
WITH __expression SELECT  
    __signal <= __expression WHEN __constant_value,  
    __expression WHEN __constant_value,  
    __expression WHEN __constant_value,  
    __expression WHEN __constant_value;
```

```
__signal <= __expression WHEN __boolean_expression ELSE  
    __expression WHEN __boolean_expression ELSE  
    __expression;
```

```
IF __expression THEN  
    __statement;  
    __statement;  
ELSIF __expression THEN  
    __statement;  
    __statement;  
ELSE  
    __statement;  
    __statement;  
END IF;
```

```
<generate_label>:  
    FOR <loop_id> IN <range> GENERATE  
        -- Concurrent Statement(s)  
    END GENERATE;
```

```
CASE __expression IS  
    WHEN __constant_value =>  
        __statement;  
        __statement;  
    WHEN __constant_value =>  
        __statement;  
        __statement;  
    WHEN OTHERS =>  
        __statement;  
        __statement;  
END CASE;
```

```
WAIT UNTIL __expression;
```

