

1. VHDL Analysis (circuit synthesis)

Given the following VHDL specification, draw the corresponding circuit.

```
ENTITY T1Prob1 IS
    PORT (sysClk : IN STD_LOGIC;
          D      : IN STD_LOGIC;
          Z      : OUT STD_LOGIC_VECTOR (4 DOWNTO 0));
END T1Prob1;

ARCHITECTURE Prob1Arch OF T1Prob1 IS
    SIGNAL tempZ : STD_LOGIC;
    SIGNAL q, x : STD_LOGIC_VECTOR(3 DOWNTO 0);

    COMPONENT altROM
        PORT ( addr      : IN STD_LOGIC_VECTOR (0 TO 3);
              CS, outEn  : IN STD_LOGIC;
              outData    : OUT STD_LOGIC_VECTOR (3 DOWNTO 0));
    END COMPONENT;

BEGIN
    PROCESS
        BEGIN
            Wait Until (sysClk'event AND sysClk = '1' );
            loop1: FOR i IN 0 TO 2 loop
                loop2: FOR j IN 0 to 2 loop
                    q(i+1) <= q(i);
                end loop;
            end loop;
            q(0) <= D;
            x <= (others =>'0');
            if q = x then
                tempZ <= '1';
            else
                tempZ <= '0';
            end if;
        END PROCESS;


        altROM PORT MAP (q, tempZ,'1', Z(4 DOWNTO 1));
        Z(0) <= tempZ;

    END Prob1Arch;
```

18 pts.

1. (continued) Put answer for Problem 1 here:

2. VHDL specification

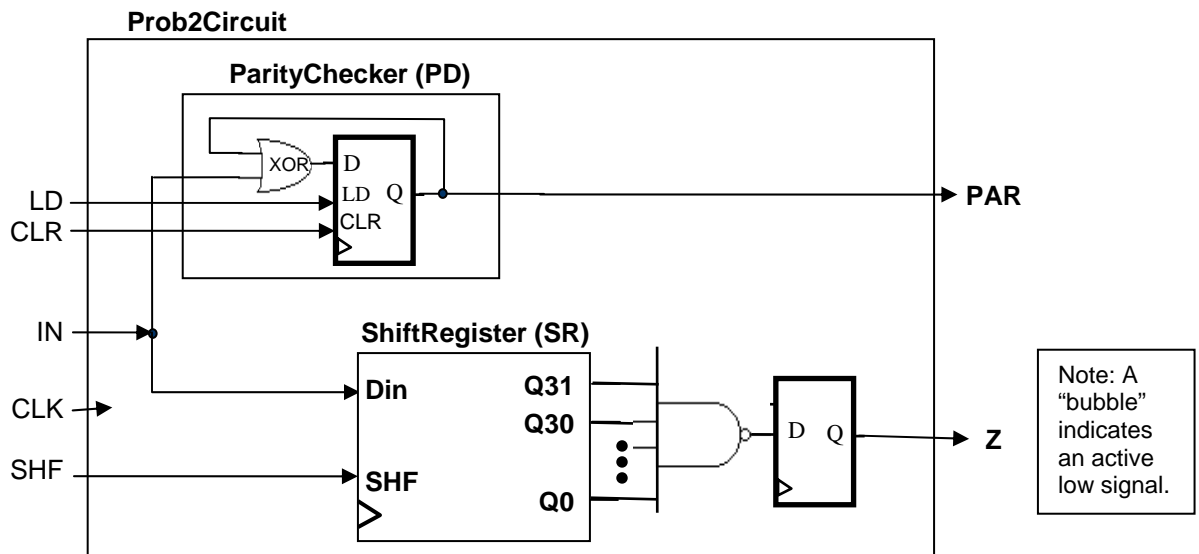

- Put your answer for Problem 2 on the next page.
- PD is a D flip-flop (and XOR gate) with synchronous LD and CLR. CLR has priority over LD.
- SR is a 32-bit shift register: If SHF = 1, it will synchronously shift right, else "hold".

18 pts.

2. **(continued)** Complete the following VHDL code to define the above circuit. All your code in the architecture **must** be inside the **one PROCESS statement**.

```
ENTITY Prob2Circuit IS
    PORT( LD, CLR, IN, CLK, SHF : IN STD_LOGIC;
          PAR, Z : OUT STD_LOGIC);
END Prob4Circuit;
```

```
ARCHITECTURE behaviorArch OF Prob4Circuit
```

```
SIGNAL
```

```
BEGIN
```



```
PROCESS (
) -- All your code must be inside this one PROCESS statement.
-- The best answer gets the most points.
```

```
END PROCESS
```

```
END behaviorArch;
```

12 pts.

  3. Using the GENERIC feature of VHDL, complete the following code that will define a “generic” component named genMUXDff shown in Figure 3(a). The generic component has “N” slices, each of which contains a D flip-flop and a 2-to-1 MUX as shown in Figure 3(b). Also, the output ZFlag is true when all the D flip-flops contain ‘0’.



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
ENTITY genMUXDff IS
    GENERIC (N: INTEGER :=8)
```

```
END genMUXDff;
ARCHITECTURE genArch OF genMUXDff IS
SIGNAL
BEGIN
```

```
    PROCESS ( ) -- All code should be inside a single
                -- PROCESS block
```


```
END PROCESS;
END genArch;
```

4. Based on on the VHDL code on the next page, complete the following timing diagrams.

24 pts.


(a) Complete the following timing diagram for X = '0'. Please show delays and go as far as you can. (12 pts.)

Specify countOut in binary

 

(a) Complete the following timing diagram for X = '1'. Please show delays and go as far as you can. (12 pts.)

Specify countOut in binary

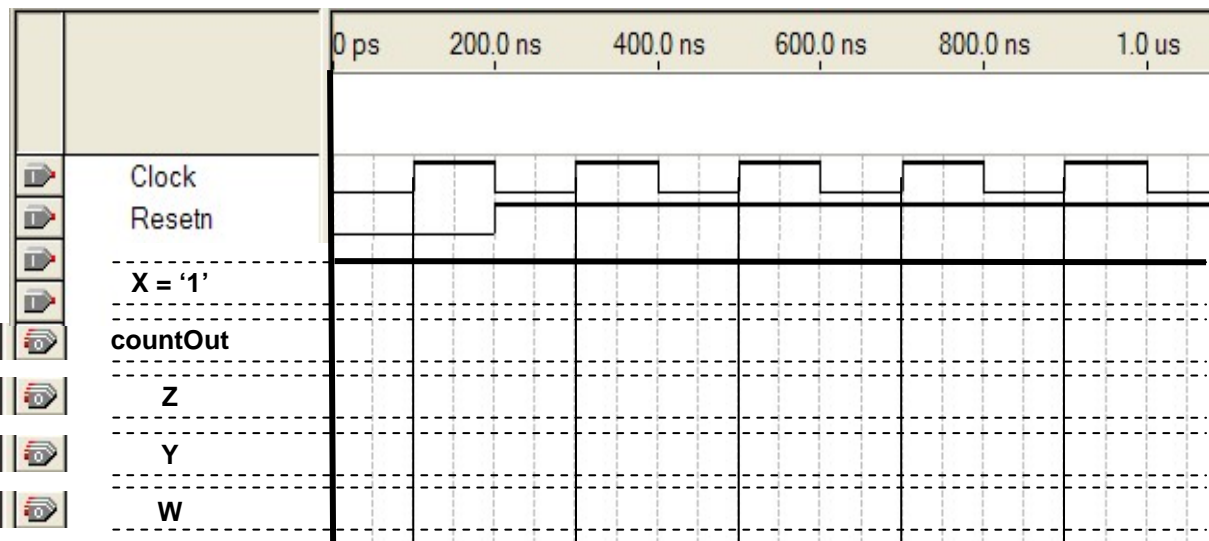

Code used for Problem 4:

```
ENTITY T1Prob4 IS
    PORT ( Clock, Resetn, X      : IN   STD_LOGIC ;
          countOut              : OUT  STD_LOGIC_Vector (1 DOWNT0 0);
          Y,Z,W                 : OUT  STD_LOGIC );
END T1Prob4 ;


ARCHITECTURE Behavior OF T1Prob4 IS
    SIGNAL count : STD_LOGIC_Vector (1 DOWNT0 0);
BEGIN
    WITH count SELECT
        W <= '1' WHEN "00",
          '1' WHEN "01",
          '0' WHEN OTHERS;

    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            count <= "01" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            Z <= '0';
            CASE count IS
                WHEN "10" =>
                    IF X = '0' THEN
                        count <= "00" ;
                        Z <= '1';
                    ELSE count <= "11" ;
                    END IF ;
                WHEN "11" =>
                    count <= "01" ;
                    Z <= '1';
                WHEN "01" =>
                    IF X = '0' THEN count <= "10";
                    ELSE count <= "00";
                    END IF ;
                WHEN "00" =>
                    count <= "10";
                    Z <= '1';
                WHEN OTHERS =>
                    count <= "10";
            END CASE ;
        END IF ;
    END PROCESS ;

    PROCESS (count, X)
    BEGIN
        CASE count IS
            WHEN "10" => Y <= '1';
            WHEN "11" => IF X = '1' THEN Y <= '1';
                        ELSE Y <= '0';
                        END IF;
            WHEN OTHERS => Y <= '0';
        END CASE;
        countOut <= count;
    END PROCESS;
END Behavior ;
```

18 pts.

5. **3-bit LCA Adder**

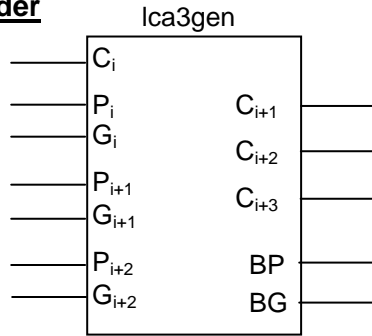

Some useful equations:

$$S_{i+1} = A_i \text{ XOR } B_i \text{ XOR } C_i$$

$$C_{i+1} = A_i \text{ AND } B_i \text{ OR } (A_i \text{ OR } B_i) \text{ AND } C_i$$


$$G_i = A_i \text{ AND } B_i$$

$$P_i = A_i \text{ OR } B_i$$









Show above is a 3-bit look-ahead carry LCA generator (lca3gen). It functions exactly like the lca2gen you designed in Lab 3, except it is a 3-bit slice.

(a) Give the necessary equations for lca3gen (in the form of sum-of-product and as a function of only the inputs (C_i , P_i , G_i , P_{i+1} , G_{i+1} , P_{i+2} , and G_{i+2}). (5 pts.)

 (b) Using 8 of the following full adder components, any number of lca3gen, and any additional gates, draw the circuit diagram of an 8-bit adder with carry lookahead (**on the next page**). (13 pts.)



        - The circuit diagram should show exactly how the components are connected. However, you can use labels when appropriate, instead of drawing the connections.



6. EEL4712 Trivia.

10 pts.

- (a) The following is the VHDL file given in the SignalTap II tutorial. Draw the corresponding circuit. Note that `RISING_EDGE(CLOCK_50)` is equivalent to `(CLOCK_50'EVENT AND CLOCK_50 = '1')` (3 pts.)

```
ENTITY switches IS
  PORT ( CLOCK_50 : IN STD_LOGIC;
        SW : IN STD_LOGIC_VECTOR(7 DOWNT0 0);
        LEDR : OUT STD_LOGIC_VECTOR(7 DOWNT0 0));
END switches;

ARCHITECTURE Behavior OF switches IS
BEGIN
  PROCESS (CLOCK_50)
  BEGIN
    IF(RISING_EDGE(CLOCK_50)) THEN
      LEDR <= SW;
    END IF;
  END PROCESS;
END Behavior;
```

Put circuit for Part (a) here.

- (b) In the SignalTap II tutorial, you were instructed to select:

- SW[7..0] as the nodes to probe
- CLOCK_50 as clock to run the SignalTap module
- SW[0] as the trigger condition and select “high” for it

After you downloaded the design onto the board, briefly explain how the SignalTap works when the analysis is run. (3 pts.)

- (c) In performance point of view, for combinatorial circuits, is it better to use a Process block or concurrent statements (e.g., WITH SELECT)? For credit, please explain. (2 pts.)

- (d) In performance point of view, for sequential circuits (e.g., registers), is it better to use a Process block or concurrent statements? For credit, please explain. (2 pts.)

```
ENTITY __entity_name IS
  PORT(__input_name, __input_name      : IN STD_LOGIC;
        __input_vector_name           : IN STD_LOGIC_VECTOR(__high downto __low);
        __bidir_name, __bidir_name     : INOUT  STD_LOGIC;
        __output_name, __output_name   : OUT    STD_LOGIC);
END __entity_name;

ARCHITECTURE a OF __entity_name IS
  SIGNAL __signal_name : STD_LOGIC;
  SIGNAL __signal_name : STD_LOGIC;
BEGIN
  -- Process Statement
  -- Concurrent Signal Assignment
  -- Conditional Signal Assignment
  -- Selected Signal Assignment
  -- Component Instantiation Statement
END a;

SIGNAL __signal_name : __type_name;

__instance_name: __component_name PORT MAP (__component_port => __connect_port,
                                              __component_port => __connect_port);

WITH __expression SELECT
  __signal <= __expression WHEN __constant_value,
              __expression WHEN __constant_value,
              __expression WHEN __constant_value,
              __expression WHEN __constant_value;

__signal <= __expression WHEN __boolean_expression ELSE
  __expression WHEN __boolean_expression ELSE
  __expression;

IF __expression THEN
  __statement;
  __statement;
ELSIF __expression THEN
  __statement;
  __statement;
ELSE
  __statement;
  __statement;
END IF;

WAIT UNTIL __expression;

CASE __expression IS
  WHEN __constant_value =>
    __statement;
    __statement;
  WHEN __constant_value =>
    __statement;
    __statement;
  WHEN OTHERS =>
    __statement;
    __statement;
END CASE;
```