

EEL 4712  
Midterm 1 – Spring 2013  
**VERSION 1**

Name: \_\_\_\_\_

UFID: \_\_\_\_\_

Sign your name here if you would like for your test to be returned in class:

\_\_\_\_\_

**IMPORTANT:**

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

**COVER SHEET:**

Problem#:	Points
1 (15 points)	
2 (12 points)	
3 (6 points)	
4 (6 points)	
5 (6 points)	
6 (6 points)	
7 (6 points)	
8 (12 points)	
9 (12 points)	
10 (15 points)	
11 (4 points)	<b>4</b>

**Total:**

**Regrade Info:**

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

__instance_name: __component_name PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

type array_type is array(__upperbound downto __lowerbound);

```

- 1) (15 points) Fill in the following behavioral VHDL to implement the illustrated circuit. Assume that `clk` and `rst` connect to every register. All wires and operations are *width* bits. Ignore overflow from the adders.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

```
entity test1 is
  generic (
    width      : positive := 16);
  port (
    clk, rst   : in  std_logic;
    in1, in2, in3 : in  std_logic_vector(width-1 downto 0);
    output     : out std_logic_vector(width-1 downto 0));
end test1;
```

```
architecture BHV of test1 is
```

```
begin
```


```
  process(clk, rst)
```

```
    begin
      if (rst = '1') then
```

```
        elsif (rising_edge(clk)) then
```

```
          end if;
        end process;
```

```
end BHV;
```

 

2) (12 points) Identify the violations (if any) of the *synthesis coding guidelines for sequential logic*.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity count is
  generic (
    width : positive := 16);
  port (
    clk   : in  std_logic;
    rst   : in  std_logic;
    en    : in  std_logic;
    input : in  std_logic_vector(width-1 downto 0);
    zero  : out std_logic);
end count;

architecture BHV of count is

  signal count : signed(width-1 downto 0);

begin

  process(clk, rst)
  begin

    if (count > 0) then
      count <= count - 1;
    end if;

    if (rst = '1') then
      count <= (others => '0');
    end if;

    elsif (clk = '1' and clk'event) then

      if (en = '1') then
        count <= signed(input);
      end if;


      if (count = 0) then
        zero <= '1';
      else
        zero <= '0';
      end if;

    end if;
  end process;
end BHV;
```


- 3) (6 points) When using sequential statements, when does a signal's value get updated?
  
  
  
  
  
  
  
  
  
  
- 4) (6 points) When using sequential statements, when does a variable's value get updated?
  
  
  
  
  
  
  
  
  
  
- 5) (6 points) For a behavioral architecture of a priority encoder, briefly explain if a *case* statement or an *if* statement is a more appropriate construct.
  
  
  
  
  
  
  
  
  
  
- 6) (6 points) While implementing a behavioral architecture for an ALU, you get a warning during synthesis about a latch being inferred for output "overflow." What does this suggest is wrong with your VHDL code?
  
  
  
  
  
  
  
  
  
  
- 7) (6 points) When defining a state machine with 100 states, you notice that a particular output *x* has a value of '0' in 95 of the states. What does this suggest that you should do to simplify your code?

- 8) (12 points) Fill in the provided code to create the illustrated structural architecture using a series of *A* components. Assume you are given the shown *A* entity, which has already been defined elsewhere. The length of the series is specified by the generic *width*.

Pre-defined Entity A

 

Desired Structural Architecture

 

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity test2 is
  generic (
    width      : positive := 8);
  port (
    x : in  std_logic_vector(width-1 downto 0);
    j : in  std_logic;
    y : out std_logic_vector(width-1 downto 0);
    z : out std_logic);
end test2;
```

architecture STR of test2 is

```
  component A
    port (
      in1, in2 : in  std_logic;
      out1, out2 : out std_logic);
  end component;
```

```
begin
  U_LOOP : for i in 0 to width-1 generate

    U_A : entity work.A
      port map (

        in1 =>

        in2 =>

        out1 =>


        out2 =>

      );

  end generate U_LOOP;
```

```
end STR;
```

 - 9) (12 points) Fill in the code to implement the following Moore finite state machine, *using the 2-process FSM model*. Assume that if an edge does not have a corresponding condition, that edge is **always taken on a rising clock edge**. Assume that S0 is the start state. Use the next page if extra room is needed.



```

library ieee;
use ieee.std_logic_1164.all;

entity fsm is
  port (
    clk, rst, go, x : in std_logic;
    y                : out std_logic_vector(1 downto 0));
end fsm;

architecture PROC2 of fsm is

  type STATE_TYPE is (S0, S1, S2, S3);
  signal state, next_state : STATE_TYPE;

begin

  process(clk, rst)
  begin
    if (rst = '1') then

      elsif (clk'event and clk = '1') then

        end if;
      end process;

  process(
    begin
  
```



```
end process;  
end PROC2;
```



10) a. (3 points) Briefly describe the tradeoffs of ripple-carry and carry-lookahead adders.

b. (3 points) Define the block propagate (BP) output of a 4-bit carry-lookahead adder in terms of the propagate signal ( $p_i$ ) of each bit  $i$ .

  c. (8 points) On the graphs below, draw the area and delay as a function of width for both ripple-carry and carry-lookahead adders. Assume the carry-lookahead adder has the ideal delay. Make sure to label each curve.



11) 4 free points for having to take a test at 8:30am.