

EEL 4712
Midterm 1 – Spring 2011
VERSION 1

Name: _____

UFID: _____

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

COVER SHEET:

Problem#:	Points
1 (5 points)	
2 (5 points)	
3 (12 points)	
4 (12 points)	
5 (16 points)	
6 (16 points)	
7 (16 points)	
8 (15 points)	
9 (3 points)	3

Total:

Regrade Info:

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

__instance_name: __component_name PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

type array_type is array(__upperbound downto __lowerbound);

```

1) (5 points) Given the following ALU entity:

```
library ieee;
use ieee.std_logic_1164.all;

entity ALU is
  generic (
    WIDTH      :    positive := 16);
  port (
    input1, input2 : in  std_logic_vector(WIDTH-1 downto 0);
    sel           : in  std_logic_vector(3 downto 0);
    output       : out std_logic_vector(WIDTH-1 downto 0));
end ALU;
```

show the corresponding value of the width generic next to each of the following instantiations:

```
UUT : alu
  generic map (width => 8)
  port map (
    input1      => input1,      Width =
    input2      => input2,
    sel         => sel,
    output      => output);
```

```
UUT2 : alu
  port map (
    input1      => input3,      Width =
    input2      => input4,
    sel         => sel2,
    output      => output2);
```

2) (5 points) True/false. If an entity doesn't specify a default value for a generic, and an instantiation of the entity does not use a generic map, then the generic defaults to 32.

- 3) (12 points) Identify the violation of the *synthesis coding guidelines for combinational logic* discussed in class (there is only one), and the effect on the synthesized circuit.

```
process(state, go)
begin

    next_state <= state;

    case state is
    when STATE_0 =>
        done <= '0';
        output <= "00";
        if (go = '1') then
            next_state <= STATE_1;
        end if;

    when STATE_1 =>
        output <= "01";
        if (go = '1') then
            next_state <= STATE_2;
        end if;

    when STATE_2 =>
        output <= "10";
        if (go = '1') then
            next_state <= STATE_3;
        end if;

    when STATE_3 =>
        done <= '1';
        output <= "11";
        if (go = '1') then
            next_state <= STATE_0;
        end if;

    when others => null;
    end case;
end process;
```

4) (12 points) For the following entity, fill in the waveform for “output” of each architecture assuming the values shown are in decimal format:

```
entity ADD is
  port (
    input1, input2 : in  std_logic_vector(15 downto 0);
    output          : out std_logic_vector(15 downto 0);
    overflow        : out std_logic);
end ADD;


architecture BHV1 of ADD is
  signal temp : unsigned(16 downto 0);
begin
  process(input1, input2)
  begin
    temp    <= unsigned("0"&input1) + unsigned("0"&input2);
    output  <= std_logic_vector(temp(15 downto 0));
    overflow <= std_logic(temp(16));
  end process;
end BHV1;

architecture BHV2 of ADD is
begin
  process(input1, input2)
  variable temp : unsigned(16 downto 0);
  begin
    temp    := unsigned("0"&input1) + unsigned("0"&input2);
    output  <= std_logic_vector(temp(15 downto 0));
    overflow <= std_logic(temp(16));
  end process;
end BHV2;

architecture BHV3 of ADD is
  signal temp : unsigned(16 downto 0);
begin
  temp    <= unsigned("0"&input1) + unsigned("0"&input2);
  output  <= std_logic_vector(temp(15 downto 0));
  overflow <= std_logic(temp(16));
end BHV3;
```

Input1	0	0	10	10	100
Input2	1	2	1	2	1
Output (BHV1)					
Output (BHV2)					
Output (BHV3)					

 - 5) (16 points) Fill in the code provided below to create a ripple carry adder with generic width. *You must use a structural architecture with the provided generate loop that connects together the full-adder (FA) components.* The circuit should look like this:



```
entity adder is
  generic (
    WIDTH : positive := 8);
  port (
    x, y : in std_logic_vector(WIDTH-1 downto 0);
    cin  : in std_logic;
    s    : out std_logic_vector(WIDTH-1 downto 0);
    cout : out std_logic);
end adder;
```

```
architecture RIPPLE_CARRY of adder is
```

```
  component fa
    port (
      x, y, cin : in std_logic;
      s, cout  : out std_logic);
  end component;
```

```
  Begin
```

```
    U_ADD : for i in 0 to WIDTH-1 generate
```

```
      U_FA : fa port map (
```

```
);
```

```
  end generate U_ADD;
```

```
end RIPPLE_CARRY;
```

- 6) (16 points) Draw a schematic for the register-transfer-level (RTL) circuit that will be synthesized from the following VHDL code. Clearly label all inputs, outputs, and show the corresponding location of internal signals.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity bhv_test is
  port (
    clk, rst      : in  std_logic;
    input1, input2 : in  std_logic_vector(7 downto 0);
    input3, input4 : in  std_logic_vector(7 downto 0);
    input5        : in  std_logic_vector(7 downto 0);
    output        : out std_logic_vector(7 downto 0));
end bhv_test;

architecture BHV of bhv_test is


  signal add1, add2, add3 : std_logic_vector(7 downto 0);
  signal delay1, delay2  : std_logic_vector(7 downto 0);

begin
  process(clk, rst)
  begin
    if (rst = '1') then
      add1  <= (others => '0');
      add2  <= (others => '0');
      add3  <= (others => '0');
      delay1 <= (others => '0');
      delay2 <= (others => '0');
    elsif (clk'event and clk = '1') then
      add1  <= std_logic_vector(unsigned(input1)+unsigned(input2));
      add2  <= std_logic_vector(unsigned(input3)+unsigned(input4));
      add3  <= std_logic_vector(unsigned(add1)+unsigned(add2));
      delay1 <= input5;
      delay2 <= delay1;
    end if;
  end process;

  output <= std_logic_vector(unsigned(add3)+unsigned(delay2));

end BHV;
```

 7) (16 points) Fill in the skeleton code to implement the following Moore finite state machine, *using the 2-process FSM model*. Use the next page if extra room is needed.



```

entity fsm is
  port (
    clk, rst, up_dn : in  std_logic;
    x                : out std_logic_vector(1 downto 0));
end fsm;

architecture TWO_PROC of fsm is

  signal state, next_state : STATE_TYPE;

begin

  process(clk, rst)
  begin

    end process;

    process(
    )
    begin
  
```



```
end process;  
end TWO_PROC;
```

- 8) a. (5 points) Define the logic for the generate and propagate bits for a single bit i of a carry-lookahead adder in terms of the x and y inputs.
- b. (5 points) Define the block propagate and block generate for a 4-bit CLA, assuming p_i is the propagate of a single bit and g_i is the generate of a single bit.
- c. (5 points) Describe the tradeoffs between a ripple-carry adder and a carry-lookahead adder.
- d. (3 extra credit points) What realistic limitation prevents a carry-lookahead adder from achieving a constant delay for any width?
- 9) (3 free points) Why do I try to avoid multiple choice questions on tests?
- a) because they are confusing
 - b) because there are multiple possible answers
 - c) because there are too many choices
 - d) because there are multiple possible answers
 - e) $a + b$
 - f) $b + c$
 - g) $a + b + c$
 - h) $b + c + d$
 - i) $a + b + c + d$
 - j) all of the above
 - k) some of the above
 - l) $b \text{ xor } c \text{ nand } h$
 - m) true
 - n) false
 - o) neither