

EEL 4712  
Midterm 1 – Spring 2019  
**VERSION 1**

Name: \_\_\_\_\_

UFID: \_\_\_\_\_

Sign here to give permission to return your test in class, where other students might see your score:

\_\_\_\_\_

**IMPORTANT:**

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

**COVER SHEET:**

Problem#:	Points
1 (25 points)	
2 (9 points)	
3 (14 points)	
4 (15 points)	
5 (5 points)	
6 (5 points)	
7 (5 points)	
8 (5 points)	
9 (12 points)	
10 (5 points)	<b>5</b>

**Total:**

**Regrade Info:**

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

```

```

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

```

```

__instance_name: __component_name
GENERIC MAP(__component_generic => __connect_generic)
PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

```

```

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

```

```

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

```

```

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

```

```

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

```

```

type array_type is array(__upperbound downto __lowerbound);

```

- 1) (25 points) Fill in the VHDL to implement the illustrated circuit. Assume that `clk` and `rst` connect to every register in the schematic. All wires/operations are *width* bits except for `in4`, which is a single bit. Ignore adder overflow. Assume the mux selects the left input when the select = '1'. Use the next page if necessary.


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity example is
  generic (width : positive := 8);
  port(
    clk, rst      : in  std_logic;
    in1, in2, in3 : in  std_logic_vector(width-1 downto 0);
    in4           : in  std_logic;
    out1         : out std_logic_vector(width-1 downto 0));
end example;

architecture BHV of example is

```

 

```

begin
  process(clk, rst)
  begin
    if (rst = '1') then

      elsif (rising_edge(clk)) then

        end if;
    end process;

```

end BHV;

- 2) (9 points) Given the two following entities *alu* and *alu\_top*:
- (3 points) Modify the generic map for *alu* instantiation in *alu\_top* to create an *alu* with a width of 7 bits.
  - (3 points) Assume that entity *alu* has 2 architectures: FAST and SMALL. Modify the *alu* instantiation in *alu\_top* to explicitly use the FAST architecture.
  - (3 points) True/False. The initialization of *width* to 4 in the *alu* entity's generic definition overrides any value specified in the generic map.

```
entity alu is
  generic (
    width : positive := 4);
  port (
    in1   : in  std_logic_vector(width-1 downto 0);
    in2   : in  std_logic_vector(width-1 downto 0);
    sel   : in  std_logic_vector(1 downto 0);
    output : out std_logic_vector(width-1 downto 0));
end alu;
```

---

```
library ieee;
use ieee.std_logic_1164.all;

entity alu_top is
  port (
    in1   : in  std_logic_vector(6 downto 0);
    in2   : in  std_logic_vector(6 downto 0);
    sel   : in  std_logic_vector(1 downto 0);
    output : out std_logic_vector(6 downto 0));
end alu_top;

architecture STR of alu_top is
begin
  U_ALU : entity work.alu
    generic map (

    )
    port map (
      in1   => in1,
      in2   => in2,
      sel   => sel,
      output => output);
end STR;
```

3) a. (10 points) Identify the violation of the synthesis coding guidelines for *combinational* logic in the following code, and state the effect on the synthesized circuit. Note: there are no syntax, casting, or width-mismatch errors.

b. (4 points) Fix the violation with a single line of code.

```
process(en, state)
begin

    case state is
        when STATE_0 =>

            output <= "0001";

            if (en = '1') then
                next_state <= STATE_1;
            end if;

        when STATE_1 =>

            output <= "0010";

            if (en = '1') then
                next_state <= STATE_2;
            end if;

        when STATE_2 =>

            output <= "0100";

            if (en = '1') then
                next_state <= STATE_3;
            end if;

        when STATE_3 =>

            output <= "1000";

            if (en = '1') then
                next_state <= STATE_0;
            end if;

        when others => null;
    end case;
end process;
```

- 4) (15 points) Fill in the provided code to create the illustrated circuit as a structural architecture using the specified FF component. Connect each FF to the clock and reset (not shown in figure). Use the next page if necessary.


```
library ieee;
use ieee.std_logic_1164.all;

entity structure is
    generic (depth : positive := 16);
    port (clk      : in  std_logic;
          rst      : in  std_logic;
          input    : in  std_logic;
          output   : out std_logic);
end structure;

architecture STR of structure is

    component ff
        port (clk, rst, D : in  std_logic;
              Q           : out std_logic);
    end component;
```

```
begin
```

 

end STR;

- 5) (5 points) Create a for loop that defines the generate (g) and propagate (p) bits for a CLA in terms of inputs x and y. Assume that g, p, x, and y are all std\_logic\_vector signals of width bits. *Note: you do not need the carry logic, just the generate and propagate.*

```
process(x, y)
begin
```

```
end process;
```

- 6) (5 points) When is it safe to use a for loop in synthesizable code (choose the best answer):
- When feedback from one register to another is required in the circuit
  - When you need to chain multiple operations into a single cycle
  - When the unrolled version of the loop corresponds to the intended circuit
  - When the number of iterations of the loop is known at compile time

- 7) (5 points) Explain why the following code will have errors during compilation/synthesis (assume the numeric\_std package is used):

```
signal x, y, z : std_logic_vector(7 downto 0);
...
x <= unsigned(y) + unsigned(z);
```

- 8) (5 points) Explain why the following code will have errors during compilation/synthesis (assume the numeric\_std package is used):

```
signal in1, in2 : unsigned(7 downto 0);
signal sum : unsigned(8 downto 0);
...
sum <= in1 + in2;
```

