

EEL 4712  
Midterm 2 – Spring 2011  
VERSION 1

Name: \_\_\_\_\_

UFID: \_\_\_\_\_

Sign your name here if you would like for your test to be returned in class:

\_\_\_\_\_

**IMPORTANT:**

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- As always, the best answer gets the most points.

**COVER SHEET:**

Problem#:	Points
1 (6 points)	
2 (6 points)	
3 (8 points)	
4 (10 points)	
5 (12 points)	
6 (6 points)	
7 (6 points)	
8 (12 points)	
9 (30 points)	
10 (4 points)	

**Total:**

*Solution*

**Regrade Info:**

**ENTITY** \_\_entity\_name **IS**

PORT(\_\_input\_name, \_\_input\_name : IN STD\_LOGIC;  
\_\_input\_vector\_name : IN STD\_LOGIC\_VECTOR(\_\_high downto \_\_low);  
\_\_bidir\_name, \_\_bidir\_name : INOUT STD\_LOGIC;  
\_\_output\_name, \_\_output\_name : OUT STD\_LOGIC);  
**END** \_\_entity\_name;

**ARCHITECTURE** a OF \_\_entity\_name **IS**

SIGNAL \_\_signal\_name : STD\_LOGIC;  
**BEGIN**

-- Process Statement  
-- Concurrent Signal Assignment  
-- Conditional Signal Assignment  
-- Selected Signal Assignment  
-- Component Instantiation Statement  
**END** a;

\_\_instance\_name: \_\_component\_name **PORT MAP** (\_\_component\_port => \_\_connect\_port,  
\_\_component\_port => \_\_connect\_port);

**WITH** \_\_expression **SELECT**

\_\_signal <= \_\_expression **WHEN** \_\_constant\_value,  
\_\_expression **WHEN** \_\_constant\_value,  
\_\_expression **WHEN** \_\_constant\_value,  
\_\_expression **WHEN** \_\_constant\_value;  
\_\_signal <= \_\_expression **WHEN** \_\_boolean\_expression **ELSE**  
\_\_expression **WHEN** \_\_boolean\_expression **ELSE**  
\_\_expression;

**IF** \_\_expression **THEN**

\_\_statement;  
\_\_statement;  
**ELSIF** \_\_expression **THEN**  
\_\_statement;  
\_\_statement;  
**ELSE**  
\_\_statement;  
\_\_statement;  
**END IF**;

**CASE** \_\_expression **IS**

**WHEN** \_\_constant\_value =>  
\_\_statement;  
\_\_statement;  
**WHEN** \_\_constant\_value =>  
\_\_statement;  
\_\_statement;  
**WHEN OTHERS** =>  
\_\_statement;  
\_\_statement;  
**END CASE**;

<generate\_label>: **FOR** <loop\_id> **IN** <range> **GENERATE**

-- Concurrent Statement(s)  
**END GENERATE**;

**type** \_\_identifier is *type\_definition*;

**subtype** \_\_identifier is *subtype\_indication*;

- 1) (5 points) Block RAMs on FPGA generally only support synchronous reads. Explain why the following code will not be inferred as block RAM, and also mention how to change the code so that block RAM is inferred during synthesis.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ram is
  port (clk      : in  std_logic;
        we       : in  std_logic;
        rd_addr  : in  std_logic_vector(4 downto 0);
        wr_addr  : in  std_logic_vector(4 downto 0);
        data_in  : in  std_logic_vector(3 downto 0);
        data_out  : out std_logic_vector(3 downto 0));
end ram;

architecture syn of ram is
  type ram_type is array (31 downto 0) of std_logic_vector (3 downto 0);
  signal RAM : ram_type;
begin
  process (clk)
  begin
    if (clk'event and clk = '1') then
      if (we = '1') then
        RAM(to_integer(unsigned(wr_addr))) <= data_in;
      end if;
    end if;
  end process;

  data_out <= RAM(to_integer(unsigned(rd_addr)));
end syn;
```

*This is an asynchronous read. To be inferred as block RAM, it should occur on the rising clock edge (i.e. synchronously).*

- 2) a. (2 points) Write a VHDL type declaration called MY\_ARRAY that creates a 2D array with 5 rows and 10 columns, where each element is a 16-bit std\_logic\_vector.

type MY\_ARRAY is array (0 to 5, 0 to 10) of std\_logic\_vector(15 downto 0);

- b. (2 points) Write a VHDL type declaration called MY\_ARRAY that creates a 2D array with unconstrained ranges for each dimension, where each element is a 16-bit std\_logic\_vector.

type MY\_ARRAY is array (natural range<>, natural range<>) of std\_logic\_vector(15 downto 0);

- c. (2 points) Using the type from part b, instantiate an object of type MY\_ARRAY with 10 rows and 20 columns.

signal example: MY\_ARRAY(0 to 10, 0 to 20);

- d. (2 points) Which of the following, if any, are legal VHDL array declarations (pre-2008)?

type MY\_ARRAY is array (natural range<>, natural range<>) of std\_logic\_vector

type MY\_ARRAY is array (natural range<>, 0 to 50) of std\_logic\_vector

type MY\_ARRAY is array (0 to 100, 0 to 50) of std\_logic\_vector

none

- 3) a. (5 points) For the VGA lab, you were required to display the image in 5 different locations. Given an image that is 128x128 and a screen resolution of 640x480, define the constants that specify the pixel boundaries when displaying the image centered vertically, but horizontally aligned with the left side of the screen. Show your work.

constant X\_START : integer := 0

constant X\_END : integer := 127


constant Y\_START : integer :=  $480/2 - 128/2 = 176$

constant Y\_END : integer :=  $480/2 + 128/2 - 1 = 303$

- b. (5 points) In class, I explained that the VGA control signals needed to be delayed to align with the output of the ROM. Explain why these signals would not be aligned without the delay registers.

The ROM uses a synchronous read, which causes a one cycle delay.

 - 4) (10 points) Map the following circuit onto 4-input, 2-output LUTs by drawing shapes around each portion of the circuit that is mapped to an individual LUT.



- 5) (5 points) What is the maximum number of gates that can be implemented in a 4-input, 2-output LUT?

- a.  $2^4$  gates
- b.  $4^2$  gates
- c.  $2^4 \cdot 2$  gates
- d.  $4^2 \cdot 2$  gates
- e. ☒ other

There is no maximum

6) (10 points) Briefly describe the purpose of each of the following components:

Switch box: connects row and column routing tracks


Connection box: connects CLB I/O to routing tracks

Routing tracks: wires used to communicate between components

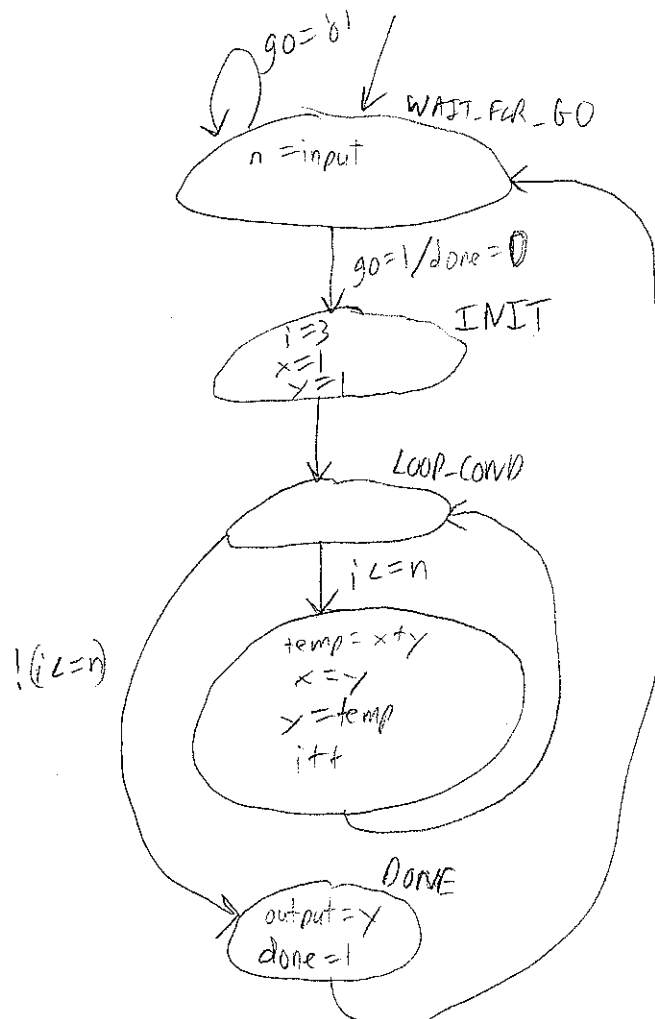7) a. (13 points) Create an FSM that implements the following pseudo-code. Do not write VHDL and instead leave the FSM in graphical form (i.e., state machine with corresponding operations in each state). Make sure to specify all operations and state transitions. Note that "input" and "output" are I/O. Assume there is also a go signal that starts the FSM (i.e. the circuit waits at the beginning until go is asserted) and a done signal that is asserted when the output is valid.

```

n = input;
i = 3;
x = 1;
y = 1;
while (i <= n) {
    temp = x+y;
    x = y;
    y = temp;
    i++;
}
output = y;
    
```



b. (13 points) Convert the previous FSM into VHDL using the 1-process FSM model:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity FSM is
  port (
    clk   : in  std_logic;
    rst   : in  std_logic;
    go     : in  std_logic;
    done   : out std_logic;
    input  : in  std_logic_vector(7 downto 0);
    output : out std_logic_vector(7 downto 0);
  );
end FSM;

architecture ONE_PROCESS of FSM is

  type state_type is (S_WAIT_FOR_GO, S_INIT, S_LOOP_COND, S_LOOP_BODY, S_DONE);
  signal state      : state_type;
  signal n, i, x, y : unsigned(7 downto 0);

begin

  process(clk, rst)
    variable temp : unsigned(7 downto 0);
  begin

    if (rst = '1') then
      state <= S_WAIT_FOR_GO;
      output <= (others => '0');
      done <= '0';
      n <= (others => '0');
      i <= (others => '0');
      x <= (others => '0');
      y <= (others => '0');

    elsif (rising_edge(clk)) then

      case state is
        when S_WAIT_FOR_GO =>

          n <= unsigned(input);

          if (go = '1') then
            done <= '0';
            state <= S_INIT;
          end if;

        when S_INIT =>

          i <= to_unsigned(3, i'length);
          x <= to_unsigned(1, i'length);
          y <= to_unsigned(1, i'length);
          state <= S_LOOP_COND;

        when S_LOOP_COND =>

          if (i <= n) then
            state <= S_LOOP_BODY;
          else
            state <= S_DONE;
          end if;
        end case;
      end process;
    end architecture;
```



```

    end if;

    when S_LOOP_BODY =>

        temp := x+y;
        x    <= y;
        y    <= temp;
        i    <= i + 1;
        state <= S_LOOP_COND;


    when S_DONE =>

        output <= std_logic_vector(y);
        done   <= '1';
        state  <= S_WAIT_FOR_GO;

    when others => null;
end case;
end if;
end process;
end ONE_PROCESS;

```

 c. (13 points) For the same pseudo-code, create a datapath capable of executing the code (ignore the controller in this step).



d. (13 points) For the datapath in the previous step, draw an FSM capable of controlling the datapath to perform the pseudo-code. In each state of the FSM, show the values of control signals that configure the FSM to do the corresponding operations.

