

EEL 4712
Midterm 1 – Spring 2016
VERSION 1

Name: _____ SOLUTION _____

UFID: _____

Sign here to give permission to return your test in class, where other students might see your score:

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

COVER SHEET:

Problem#:	Points
1 (16 points)	
2 (6 points)	
3 (16 points)	
4 (16 points)	
5 (5 points)	
6 (16 points)	
7 (6 points)	
8 (16 points)	
9 (3 points)	3

Total:

Regrade Info:

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

__instance_name: __component_name PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

type array_type is array(__upperbound downto __lowerbound);

```

- 1) (16 points) Fill in the following VHDL to implement the illustrated circuit. Assume that `clk` and `rst` connect to every register. All wires/operations are *width* bits. Ignore adder overflow.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity example is
  generic (
    width : positive := 16);
  port (
    clk,rst      : in  std_logic;
    in1, in2, in3, in4 : in  std_logic_vector(width-1 downto 0);
    out1, out2    : out std_logic_vector(width-1 downto 0));
end example;

```

architecture BHV of example is

```

    signal reg_in1, reg_in2, reg_in3, reg_in4 : unsigned(width-1 downto 0);
    signal sum_no_reg                        : unsigned(width-1 downto 0);

```

```

begin
  process(clk, rst)
  begin
    if (rst = '1') then

      reg_in1 <= (others => '0');
      reg_in2 <= (others => '0');
      reg_in3 <= (others => '0');
      reg_in4 <= (others => '0');
      out1    <= (others => '0');
      out2    <= (others => '0');

    elsif (clk'event and clk = '1') then


      reg_in1 <= unsigned(in1);
      reg_in2 <= unsigned(in2);
      reg_in3 <= unsigned(in3);
      reg_in4 <= unsigned(in4);
      out1    <= std_logic_vector(reg_in1 + reg_in2);
      out2    <= std_logic_vector(sum_no_reg + reg_in4);

    end if;
  end process;

  sum_no_reg <= reg_in2 + reg_in3;

end BHV;

```

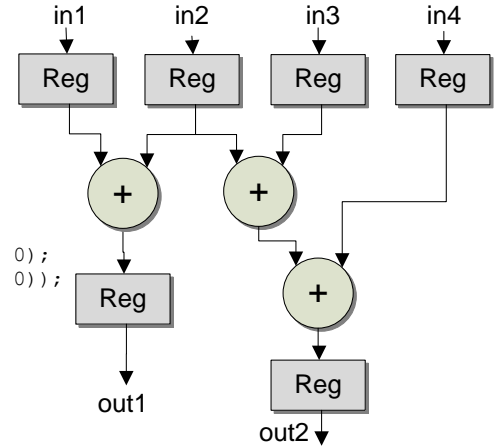

2) (6 points) Given the following entity, specify the widths of each instantiation in parts a-c.

```
entity test is
  generic (
    width : positive := 32);
  port (
    in1    : in  std_logic_vector(width-1 downto 0);
    in2    : in  std_logic_vector(width-1 downto 0);
    output : out std_logic_vector(width-1 downto 0));
end test;
```

a.

```
U_A : entity work.test
      generic map (width => 16)
      port map (in1 => in1,
                in2 => in2,
                output => output);
```

16

b.

```
U_B : entity work.test
      port map (in1 => in1,
                in2 => in2,
                output => output);
```

32

c. When entity test is used as the top-level entity.

32

3) (16 points) Fill out the outputs of the waveform for the following two architectures. Assume the left column is the start of the simulation.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mult is
  generic(
    width : positive := 16);
  port (
    input1, input2 : in  std_logic_vector(width-1 downto 0);
    output          : out std_logic_vector(width-1 downto 0);
    overflow        : out std_logic);
end mult;

architecture BHV1 of mult is

  signal temp : unsigned(2*width-1 downto 0);
begin
  process(input1, input2)
  begin
    temp <= unsigned(input1) * unsigned(input2);
    output <= std_logic_vector(temp(width-1 downto 0));

    if (temp(2*width-1 downto width) = 0) then
      overflow <= '0';
    else
      overflow <= '1';
    end if;
  end process;
end BHV1;
```

input1	1	2	3	4
input2	10	5	3	5
output	U	10	10	9
overflow	U	0	0	0

```
architecture BHV2 of mult is
begin
  process(input1, input2)
  variable temp : unsigned(2*width-1 downto 0);
  begin
    temp := unsigned(input1) * unsigned(input2);
    output <= std_logic_vector(temp(width-1 downto 0));

    if (temp(2*width-1 downto width) = 0) then
      overflow <= '0';
    else
      overflow <= '1';
    end if;
  end process;
end BHV2;
```

input1	1	2	3	4
input2	10	5	3	5
output	10	10	9	20
overflow	0	0	0	0

- 4) (16 points points) **a.** Identify any violations of the *synthesis coding guidelines for combinational logic* and **b.** specify the effect on the synthesized circuit.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mult is
  generic(
    width : positive := 16);
  port (
    input1, input2 : in  std_logic_vector(width-1 downto 0);
    output          : out std_logic_vector(width-1 downto 0);
    overflow        : out std_logic);
end mult;

architecture BHV4 of mult is
begin
  process(input1, input2)
    variable temp : unsigned(2*width-1 downto 0);
  begin
    temp := unsigned(input1) * unsigned(input2);
    output <= std_logic_vector(temp(width-1 downto 0));

    if (temp(2*width-1 downto width) /= 0) then
      overflow <= '1';
    end if;
  end process;
end BHV4;
```

- a. Overflow isn't specified on the else path**
b. Infers a latch

- 5) (5 points) The following code is correct and will synthesize to combinational logic, but what suggestion does it not follow?

```
architecture BHV3 of mult is
  signal temp : unsigned(2*width-1 downto 0) := (others => '0');
begin
  temp <= unsigned(input1) * unsigned(input2);
  output <= std_logic_vector(temp(width-1 downto 0));

  process(temp)
  begin
    if (temp(2*width-1 downto width) = 0) then
      overflow <= '0';
    else
      overflow <= '1';
    end if;
  end process;
end BHV3;
```

Signals and variables should not be initialized in synthesizable code.

- 6) (16 points) Fill in the provided code to create the illustrated structural architecture using a series of pre-existing *ff* and *mux2x1* components. Use the component declarations to determine their I/O. Note that there are a total of *width* registers and *width-1* muxes. The shift input acts as the select for all muxes.

```

library ieee;
use ieee.std_logic_1164.all;

entity test is
    generic(width : positive := 8);
    port (
        clk, rst, shift, input : in  std_logic;
        output                  : out std_logic);
end test;

architecture STR of test is

    component ff
        port (
            clk, rst, D : in  std_logic;
            Q           : out std_logic);
    end component;

    component mux2x1
        port (
            in1, in2, sel : in  std_logic;
            output        : out std_logic);
    end component;

    signal q : std_logic_vector(width-1 downto 0);
    signal mux_out : std_logic_vector(width-1 downto 1);

begin

    U_FF0 : ff port map (
        clk => clk,
        rst => rst,
        d   => input,
        q   => q(0)
    );

    U_FFS : for i in 1 to width-1 generate

        U_FF : ff port map (
            clk => clk,
            rst => rst,
            d  => mux_out(i),
            q  => q(i)
        );


        U_MUX : mux2x1 port map (
            in1  => input,
            in2  => q(i-1),
            sel  => shift,
            output => mux_out(i)
        );

    end generate U_FFS;

    output <= q(width-1);

end STR;

```

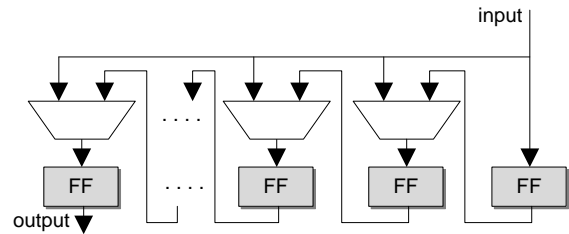

7) a. (2 points) What is the propagation delay of operations during a functional simulation?

0

b. (2 points) What file represents the vhdl for a synthesized circuit used in timing simulations?

VHO

c. (2 points) What file specifies propagation delays of signals during timing simulations?

SDO

8) a. (9 points) Define the logic for the first 3 carry outs (c_1 to c_3) of a carry lookahead adder (CLA) in terms of the propagate signals (p_i), generate signals (g_i), and carry in (c_0).

$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

$$c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$$

b. (2 points) Define the propagate signal (p_i) in terms of adder inputs x_i and y_i .

$$p_i = x_i \oplus y_i$$

c. (2 points) Define the generate signal (g_i) in terms of adder inputs x_i and y_i .

$$g_i = x_i \text{ and } y_i$$

d. (3 points) True/false. Adding extra levels of carry lookahead logic trades off propagation delay for reduced area compared to a single-level carry lookahead adder.

true

9) 3 free points for having to take a test at 8:30am.