

Name: _____

UFID: _____

Sign here to give permission to return your test in class, where other students might see your score:

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

COVER SHEET:

Problem#:	Points
1 (15 points)	
2 (4 points)	
3 (5 points)	
4 (5 points)	
5 (5 points)	
6 (4 points)	
7 (4 points)	
8 (4 points)	
9 (5 points)	
10 (12 points)	
11 (15 points)	
12 (4 points)	
13 (13 points)	
14 (5 points)	5

Total:

Regrade Info:

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

```

```

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

```

```

__instance_name: __component_name
GENERIC MAP(__component_generic => __connect_generic)
PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

```

```

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

```

```

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

```

```

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

```

```

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

```

```

type array_type is array(__upperbound downto __lowerbound);

```

- 1) (15 points) Fill in the VHDL to implement the illustrated circuit. Assume that clk and rst connect to every register in the schematic. All wires/operations are *width* bits. Ignore adder overflow.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity example is
  generic (
    width : positive := 16);
  port (
    clk,rst      : in  std_logic;
    in1, in2, in3 : in  std_logic_vector(width-1 downto 0);
    out1, out2, out3 : out std_logic_vector(width-1 downto 0));
end example;

architecture BHV of example is

  signal regIn1, regAddOut, addOut : std_logic_vector(width-1 downto 0);
begin

  process(clk, rst)
  begin
    if (rst = '1') then
      regIn1    <= (others => '0');
      regAddOut <= (others => '0');
      out1      <= (others => '0');
      out2      <= (others => '0');

    elsif (rising_edge(clk)) then


      regIn1    <= in1;
      regAddOut <= std_logic_vector(unsigned(in2)+unsigned(in3));
      out2      <= regAddOut;
      out1      <= std_logic_vector(unsigned(addOut)+unsigned(regAddOut));

    end if;
  end process;

  addOut <= std_logic_vector(unsigned(regIn1)+unsigned(in2));
  out3   <= regAddOut;

end BHV;

```

 

NOTE: There are many possible answers

- 2) (4 points) When an entity with generics is used as the top-level entity for synthesis, what values does the synthesis tool use for the generics?

The default values for each generic.

- 3) (5 points) Briefly explain why you should not initialize signals in synthesizable code.

Initializing a signal doesn't always make sense in hardware (e.g., a wire), and can cause differences between synthesis and simulation.

- 4) (5 points) Complete the following waveform. Pay close attention to the sensitivity list of the process.

```
entity alu is
    generic (
        width : positive := 8);
    port (
        in1, in2 : in  std_logic_vector(width-1 downto 0);
        sel      : in  std_logic;
        output   : out std_logic_vector(width-1 downto 0));
end alu;

architecture BHV of alu is
begin
    process(in1, in2)
    begin
        case sel is
            when '0' =>
                output <= std_logic_vector(unsigned(in1)+unsigned(in2));
            when '1' =>
                output <= std_logic_vector(unsigned(in1)-unsigned(in2));
            when others => null;
        end case;
    end process;
end BHV;
```

input1	5	5	15	15	2
input2	5	5	5	5	4
sel	'0'	'1'	'1'	'0'	'0'
output	10	10	10	10	6

Note that the process does not re-execute when only the select value changes, so the output doesn't change.

- 5) (5 points) For signals assigned using sequential statements inside a process, when does the signal get updated with the value from the assignment?

At the end of the process.

- 6) (4 points) **True/false.** Testbenches should follow the same synthesis coding as other entities.

False, testbenches are not synthesized so you can use any constructs you want.

- 7) (4 points) **True/false.** Sequential statements inside a process can reassign a signal any number of times.

true

- 8) (4 points) **True/false.** Concurrent statements can reassign a signal any number of times.

False

- 9) (5 points) Assuming you use a variable solely to get an immediately updated value, what will type of hardware resource will be synthesized?

A wire

10) (12 points points) **a.** Identify any violations of the *synthesis coding guidelines for combinational logic* and **b.** specify the effect on the synthesized circuit.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity alu is
  generic (
    width : positive := 8);
  port (
    in1, in2 : in  std_logic_vector(width-1 downto 0);
    sel      : in  std_logic;
    output   : out std_logic_vector(width-1 downto 0);
    neg      : out std_logic);
end alu;

architecture BHV of alu is
begin
  process(sel)
    variable temp : std_logic_vector(width-1 downto 0);
  begin
    case sel is
      when '0' =>
        output <= std_logic_vector(signed(in1)+signed(in2));
      when '1' =>
        temp    := std_logic_vector(signed(in1)-signed(in2));
        neg     <= temp(width-1);
        output <= temp;
      when others => null;
    end case;
  end process;
end BHV;
```

- a) Sensitivity list does not have all inputs, and *neg* isn't defined on all paths through the process**
- b) A latch will be inferred for not defining *neg* on all paths**

11) (15 points) Fill in the provided code to create the illustrated structural architecture using the specified *add* and *mul* components.

```

library ieee;
use ieee.std_logic_1164.all;

entity structure is
    generic (width : positive := 16);
    port (in1, in2, in3, in4 : in std_logic_vector(width-1 downto 0);
          output : out std_logic_vector(2*width-1 downto 0));
end structure;

architecture STR of structure is
    component add
        generic (width : positive);
        port (in1, in2 : in std_logic_vector(width-1 downto 0);
              output : out std_logic_vector(width-1 downto 0));
    end component;


    component mul
        generic (width : positive);
        port (in1, in2 : in std_logic_vector(width-1 downto 0);
              output : out std_logic_vector(2*width-1 downto 0));
    end component;

    signal mulOut1, mulOut2 : std_logic_vector(2*width-1 downto 0);
begin
    U_MUL1 : entity work.mul
        generic map (width => width)
        port map (in1 => in1,
                  in2 => in2,
                  output => mulOut1);

    U_MUL2 : entity work.mul
        generic map (width => width)
        port map (in1 => in3,
                  in2 => in4,
                  output => mulOut2);

    U_ADD : entity work.add
        generic map (width => 2*width)
        port map (in1 => mulOut1,
                  in2 => mulOut2,
                  output => output);
end STR;

```

 

12) a. (2 points) What information is provided by an sdo file?

Propagation delays

b. (2 points) How is a vho file different than a normal vhd file?

The vho represents the synthesized circuit.

13) a. (8 points) Define the logic for the carry out c_4 of a carry look-ahead adder (CLA) in terms of the propagate signals (p_i), generate signals (g_i), and carry in (c_0).

$$C4 = g3 + p3g2 + p3p2g1 + p3p2p1g0 + p3p2p1p0c0$$

b. (1 point) **True/false.** The delay of a ripple-carry adder increases linearly with width.

true

c. (1 point) **True/false.** Ignoring fan-in limitations, a CLA has a constant delay for any width.

true

d. (1 point) **True/false.** Ignoring fan-in limitations, a two-level CLA has a constant delay for any width.

true

e. (1 point) **True/false.** Ignoring fan-in limitations, a hierarchical CLA has a constant delay for any width.

false

f. (1 point) **True/false.** The delay of an adder that uses a ripple-carry connection between CLA blocks increases linearly with width.

true. It actually follows a stepwise increase for each new CLA block, but each step is linear.

14) 5 free points for having to take a test at 8:30am.