

EEL 4712
Midterm 2 – Spring 2018
VERSION 1

Name: _____

UFID: _____

Sign here to give permission for your test to be returned in class, where others might see your score:

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

COVER SHEET:

Problem#:	Points
1 (12 points)	
2 (8 points)	
3 (16 points)	
4 (20 points)	
5 (20 points)	
6 (20 points)	
Free	4

Total:

Regrade Info:

1. a. (4 points) In the VGA lab, the ROM stored blocks that were displayed as 2x2 pixels to the screen. For blocks consisting of 16x16 pixels, show the row and column addressing logic as a function of the h_count and v_count for an image that is displayed at the top-left of the screen.

Row addr = v_count / 16

Col addr = h_count / 16

- b. (4 points) Briefly describe the purpose of the horizontal sync signal in the VGA lab.

To control the drawing of individual rows

- c. (4 points) What is the purpose of a MIF file?

To initialize RAM/ROM contents

2. (8 points) You are designing a circuit that controls a display with a signal similar to h_sync in the VGA lab. This signal must be held low for 1.1 μ s (1100 ns) and then high for 5.2 μ s (5200 ns), which then repeats indefinitely. For a 50 MHz clock, show the corresponding counter values for the rising edge and falling edge of the signal. Assume that a timer value of 0 corresponds to the beginning of the low section.

50 MHz clock = 20 ns clock period

Rising edge count = 1100/20 = 55

Falling edg count = (1100+5200) / 20 = 315

3. a. (4 points) What is the relationship between number of inputs and the number of SRAM bits in a LUT? Assume a single output.

Exponential, 2^i

- b. (4 points) Other than the reconfigurable interconnect, *name* three resources provided by existing FPGAs.

DSPs, LUTs, CLBs, block RAM, I/O, PCIe, clock trees, serial transceivers


- c. (4 points) The carry chain between LUTs in a CLB is frequently used for what type of resource?

Ripple carry adder

- d. (4 points) Why do CLBs provide a mux to select between a FF and a LUT output?

To support both combinational and sequential logic

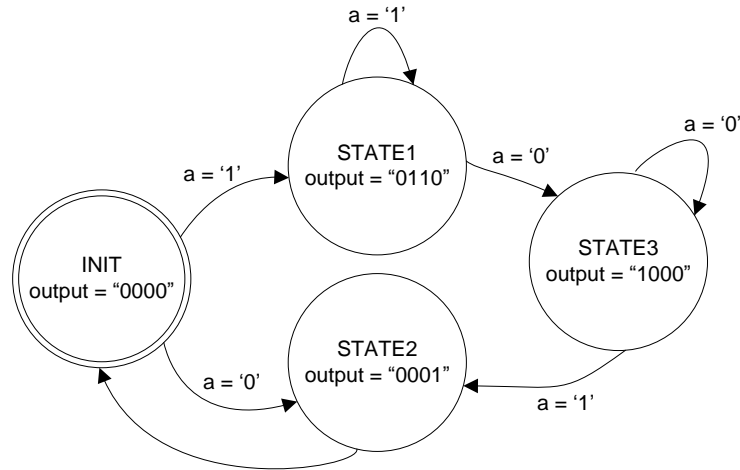4. (20 points) Fill in the code to implement the following Moore finite state machine (FSM) *using the 2-process FSM model*. **Assume that INIT is the initial state. Transitions without conditions are always taken.** Use the next page if extra room is needed.



```

library ieee;
use ieee.std_logic_1164.all;

entity fsm is
  port (
    clk, rst : in std_logic;
    a         : in std_logic;
    output    : out std_logic_vector(3 downto 0)
  );
end fsm;

architecture PROC2 of fsm is

  type STATE_TYPE is (INIT, STATE1, STATE2, STATE3);
  signal state, next_state : STATE_TYPE;

begin

  process(clk, rst)
  begin
    if (rst = '1') then
      state <= INIT;
    elsif (rising_edge(clk)) then
      state <= next_state;
    end if;
  end process;

  process(state, a)
  begin

    next_state <= state;

    case state is
      when INIT =>
        output <= "0000";
        if (a = '1') then
          next_state <= STATE1;
        else
          next_state <= STATE2;
        end if;

      when STATE1 =>
        if (a = '1') then
          next_state <= STATE1;
        else
          next_state <= STATE3;
        end if;

      when STATE3 =>
        if (a = '0') then
          next_state <= STATE3;
        else
          next_state <= STATE2;
        end if;

      when STATE2 =>
        if (a = '0') then
          next_state <= INIT;
        else
          next_state <= STATE2;
        end if;
    end case;
  end process;
end PROC2;

```

```

        output      <= "0110";
        if (a = '0') then
            next_state <= STATE3;
        end if;

    when STATE2 =>
        output      <= "0001";
        next_state <= INIT;

    when STATE3 =>
        output      <= "1000";
        if (a = '1') then
            next_state <= STATE2;
        end if;

    end case;
end process;

end PROC2;end PROC2;

```

5. (20 points) Create an FSM that implements the following pseudo-code. **Do not write VHDL and instead leave the FSM in graphical form** (i.e., state machine with corresponding operations in each state).

Inputs: go (std_logic), N (std_logic_vector)
Outputs: result (std_logic_vector), done (std_logic)

```
// reset values for outputs
done = 0; result = 0;
```


```
while (1) {
```

```
    while (go == 0);
    done = 0;
```



```
    x = 0;
    i = 1;
    nReg = N; // store input N into a register
```

```
    while (i <= nReg) {
        x = x + (2*i) - 1;
        i = i + 1;
    }
```
 
```
    result = x;
    done = 1;
    while (go == 1);
}
```



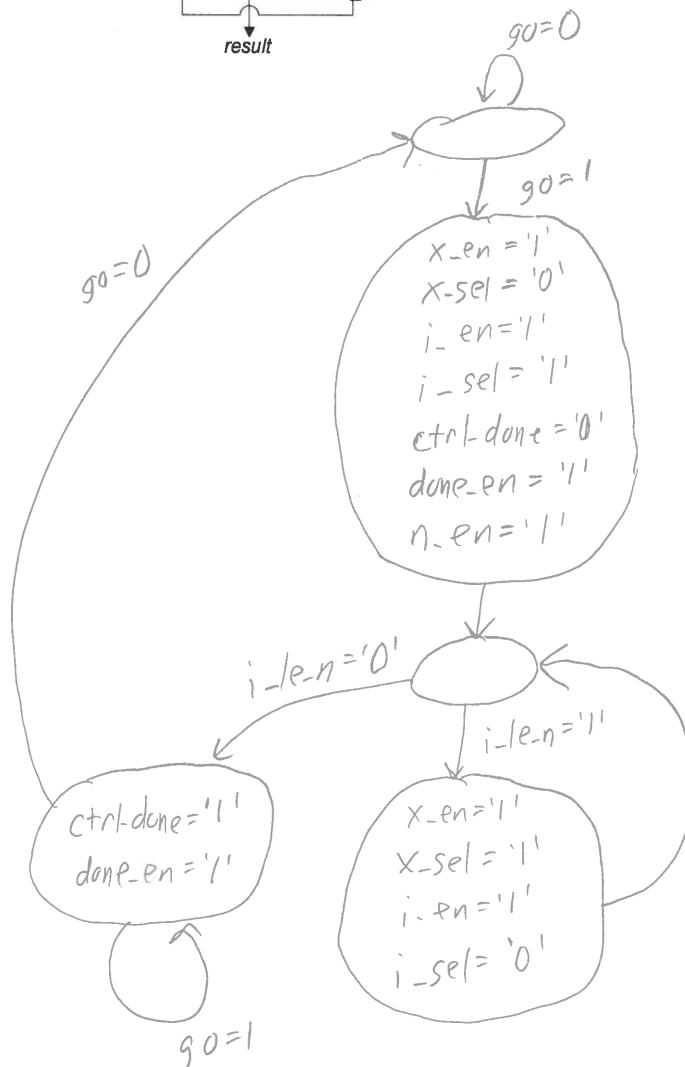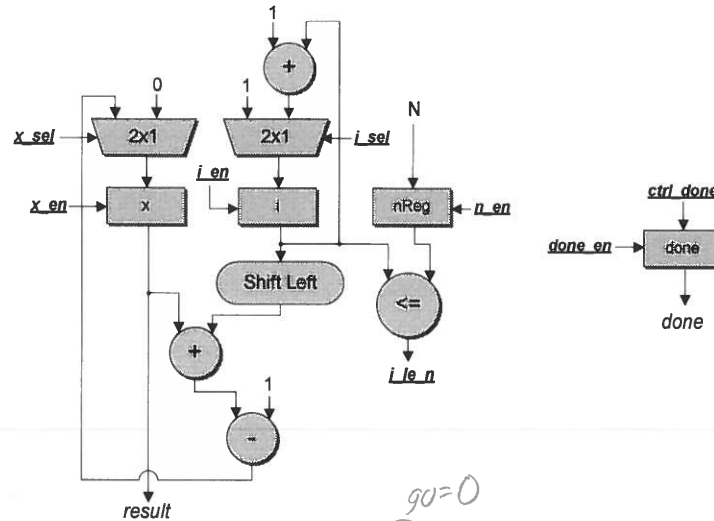6. (20 points) Draw an FSM capable of controlling the illustrated datapath to perform the pseudo-code in question 5, by assigning or reading from the underlined control signals. The controller should have an additional input for *go* (not shown in the datapath). Note that the controller specifies the done status through *ctrl_done*, but that the datapath connects this signal to the actual done output. Assume that left mux inputs have a select value of 1. **Do not write any VHDL code**, just show the FSM and control signals. Be sure to mention default signal values to save space. NOTE: this FSM might have different states than your FSMD in problem 5.



default values
 all en = '0'
 all sel = '0'
 ctrl_done = '0'