

Name: _____

UFID: _____

Sign here to give permission to return your test in class, where other students might see your score:

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- **As always, the best answer gets the most points.**

COVER SHEET:

Problem#:	Points
1 (25 points)	
2 (12 points)	
3 (15 points)	
4 (18 points)	
5 (12 points)	
6 (5 points)	
7 (4 points)	
8 (4 points)	
9 (5 points)	5

Total:

Regrade Info:

```

ENTITY __entity_name IS
PORT(__input_name, __input_name : IN STD_LOGIC;
__input_vector_name : IN STD_LOGIC_VECTOR(__high downto __low);
__bidir_name, __bidir_name : INOUT STD_LOGIC;
__output_name, __output_name : OUT STD_LOGIC);
END __entity_name;

```

```

ARCHITECTURE a OF __entity_name IS
SIGNAL __signal_name : STD_LOGIC;
BEGIN
-- Process Statement
-- Concurrent Signal Assignment
-- Conditional Signal Assignment
-- Selected Signal Assignment
-- Component Instantiation Statement
END a;

```

```

__instance_name: __component_name
GENERIC MAP(__component_generic => __connect_generic)
PORT MAP (__component_port => __connect_port,
__component_port => __connect_port);

```

```

WITH __expression SELECT
__signal <= __expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value,
__expression WHEN __constant_value;
__signal <= __expression WHEN __boolean_expression ELSE
__expression WHEN __boolean_expression ELSE
__expression;

```

```

IF __expression THEN
__statement;
__statement;
ELSIF __expression THEN
__statement;
__statement;
ELSE
__statement;
__statement;
END IF;

```

```

CASE __expression IS
WHEN __constant_value =>
__statement;
__statement;
WHEN __constant_value =>
__statement;
__statement;
WHEN OTHERS =>
__statement;
__statement;
END CASE;

```

```

<generate_label>: FOR <loop_id> IN <range> GENERATE
-- Concurrent Statement(s)
END GENERATE;

```

```

type array_type is array(__upperbound downto __lowerbound);


```

- 1) (25 points) Fill in the VHDL to implement the illustrated circuit. Assume that `clk` and `rst` connect to every register in the schematic. All wires/operations are *width* bits. Ignore adder overflow.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity example is
  generic (width : positive := 8);
  port(
    clk, rst      : in  std_logic;
    in1, in2, in3 : in  std_logic_vector(width-1 downto 0);
    out1          : out std_logic_vector(width-1 downto 0));
end example;

architecture BHV of example is
```

 

```
begin
```

```
  process(clk, rst)
  begin
    if (rst = '1') then
```

```
      elsif (rising_edge(clk)) then
```

```
      end if;
    end process;
```

```
end BHV;
```

- 2) (12 points) Fill in the VHDL to implement a simple testbench for the specified mux component. **The testbench should instantiate a mux using an architecture IF_STATEMENT.** The testbench should test 3 separate input combinations, waiting 10 ns in between tests. The testbench does *not* need to verify the correct output. Declare all signals as std_logic.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mux_tb is
end mux_tb;

architecture TB of mux_tb is

begin -- TB

    UUT : entity work.mux(
        port map (
            in1 => in1,
            in2 => in2,
            sel => sel,
            output => output);

    process
    begin

        wait;
    end process;
end TB;
```

3) a. (12 points) Identify the violation of the synthesis coding guidelines for *combinational* logic in the following priority encoder code, and state the effect on the synthesized circuit. Note: there are no syntax, casting, or width-mismatch errors.

b. (3 points) Fix the violation with a single line of code.

```
library ieee;
use ieee.std_logic_1164.all;

entity pe is
    port (
        input : in std_logic_vector(3 downto 0);
        output : out std_logic_vector(1 downto 0);
        valid : out std_logic
    );
end pe;

architecture default of pe is
begin

    process(input)
    begin

        if (input(3) = '1') then
            output <= "11";

        elsif (input(2) = '1') then
            output <= "10";

        elsif (input(1) = '1') then
            output <= "01";

        elsif (input(0) = '1') then
            output <= "00";

        else
            output <= "00";
            valid <= '0';
        end if;

    end process;

end default;
```

- 4) (18 points) Fill in the provided code to create the illustrated circuit as a structural architecture using the specified reg and add components. Connect each reg to the clock and reset (not shown in figure). All reg and add instances should use the *width* of the *structure* entity. Use the next page if necessary.

```
library ieee;
use ieee.std_logic_1164.all;
```


```
entity structure is
    generic (width : positive := 16);
    port (clk      : in  std_logic;
          rst      : in  std_logic;
          in1, in2 : in  std_logic_vector(width-1 downto 0);
          output    : out std_logic_vector(width-1 downto 0));
end structure;
```

```
architecture STR of structure is
```

```
    component reg
        generic (width : positive := 8);
        port (clk, rst : in  std_logic;
              input    : in  std_logic_vector(width-1 downto 0);
              output   : out std_logic_vector(width-1 downto 0));
    end component;
```

```
    component add
        generic (width : positive := 8);
        port (in1, in2 : in  std_logic_vector(width-1 downto 0);
              output   : out std_logic_vector(width-1 downto 0));
    end component;
```

```
begin
```

 

end STR;

5) (12 points)

- a. (3 points) Resources grow _____ with width for a carry lookahead adder.
- b. (3 points) **True/false.** Due to fan-in limitations, carry lookahead adders tend to have a latency that increases quadratically with width.
- c. (3 points) **True/false.** A ripple-carry adder using blocks of carry-lookahead adders instead of full adders has a delay that increases logarithmically with width.
- d. (3 points) Define the logic for the carry out c_4 of a carry look-ahead adder (CLA) in terms of the propagate signals (p_i), generate signals (g_i), and carry in (c_0).

6) (5 points) For the following process, what will the values of x and y be at the end of the process when $x = 20$, $y = 30$, and the process is triggered by $in1$ becoming 50? Explain your answer for partial credit.

```
signal x, y, in1 : unsigned(7 downto 0);  
...  
process(in1)  
begin  
    x <= in1 + 10;  
    y <= x + 10;  
end process;
```

- 7) (4 points) **True/false.** A single assignment to all outputs at the beginning of a process for combinational logic will guarantee there are no latches for that logic.
- 8) (4 points) **True/false.** Multiple concurrent assignments to a signal are not synthesizable, but it is valid to assign the same signal sequentially inside a process and concurrently outside a process.
- 9) 5 free points for having to take a test at 8:30am.